

Inf2C - Computer Systems

Lecture 12


Processor Design – Multi-Cycle

Boris Grot


School of Informatics
University of Edinburgh



Previous lecture: single-cycle processor

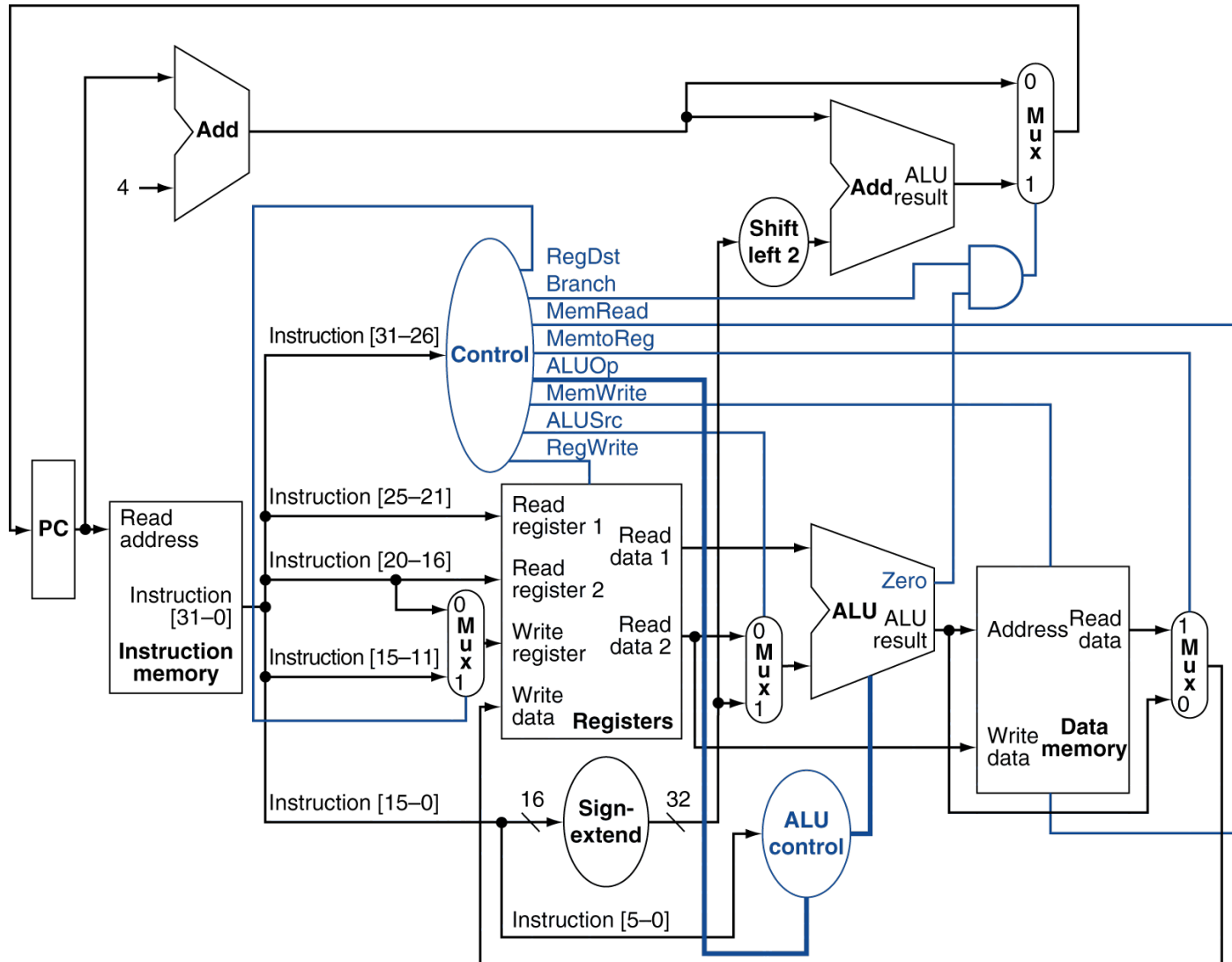

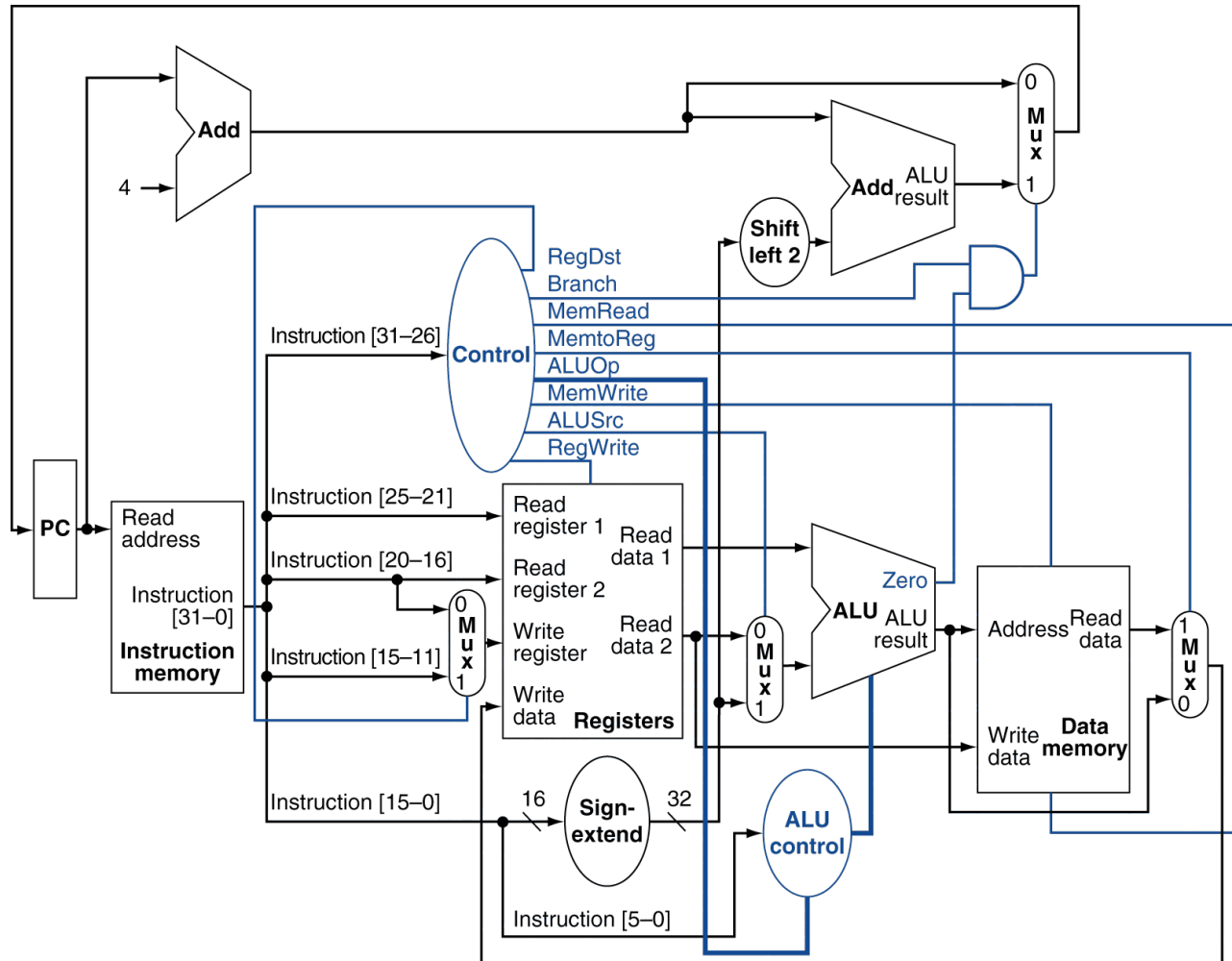Question: which instruction takes the most time to complete in a single-cycle processor?



Motivating a multi-cycle processor

Aren't single cycle processors good enough?

No!

- Speed: cycle time must be long enough for the most complex instruction to complete
 - But the average instruction needs less time
- Cost: functional units (e.g. adders) cannot be re-used within one instruction's execution

Measuring processor speed

Execution time is

$$\begin{array}{c} \text{instruction count} \\ \times \\ \text{cycles per instruction} \\ \times \\ \text{cycle time} \end{array}$$

**Programmer,
compiler, ISA**

**Processor
design**




Multi-cycle processor: Basic idea

- Break up the execution of each instruction into multiple cycles
- Reuse a common set of datapath and control components across cycles
- Ensure that the actions performed within each cycle are “generic” – i.e., common to many instructions

End result: no instruction takes more time or uses more functional units than required

Multi-cycle processor: Datapath building blocks

   - One memory
 - Shared between instructions and data
 - Common interface
- Registers
 - Read early in instruction execution
 - Written late (if ever) in inst. execution
- One ALU
 - All PC calculations (conditional & unconditional)
 - All arithmetic (inc. branch condition evaluation)



Multi-cycle processor: Basic operation

- Each instruction takes multiple cycles to execute
 - Each cycle, at least one basic function performed (e.g., Fetch or Read Registers)
 - Multiple functions can be performed in one cycle if they use different functional units
 - E.g., Fetch \rightarrow memory, PC+4 \rightarrow ALU
- Example execution: SW
 - cycle 1: Fetch (access memory)
 - cycle 2: Read registers
 - cycle 3: Compute address (use ALU)
 - cycle 4: Perform store (access memory)

Same memory,
accessed in
different cycles




Multi-cycle processor: Details

- Cycle time determined by the propagation delay through the slowest functional unit
- Number of cycles varies for different instructions
- At the end of each cycle, data required in subsequent cycles must be stored somewhere
 - Data used by subsequent instructions stored in memory and registers → same as single-cycle processor
 - Data for the current instruction stored in special registers not visible to the programmer → NEW!

Multi-cycle datapath (overview)


One memory for both Instruction & Data

One ALU for all arithmetic

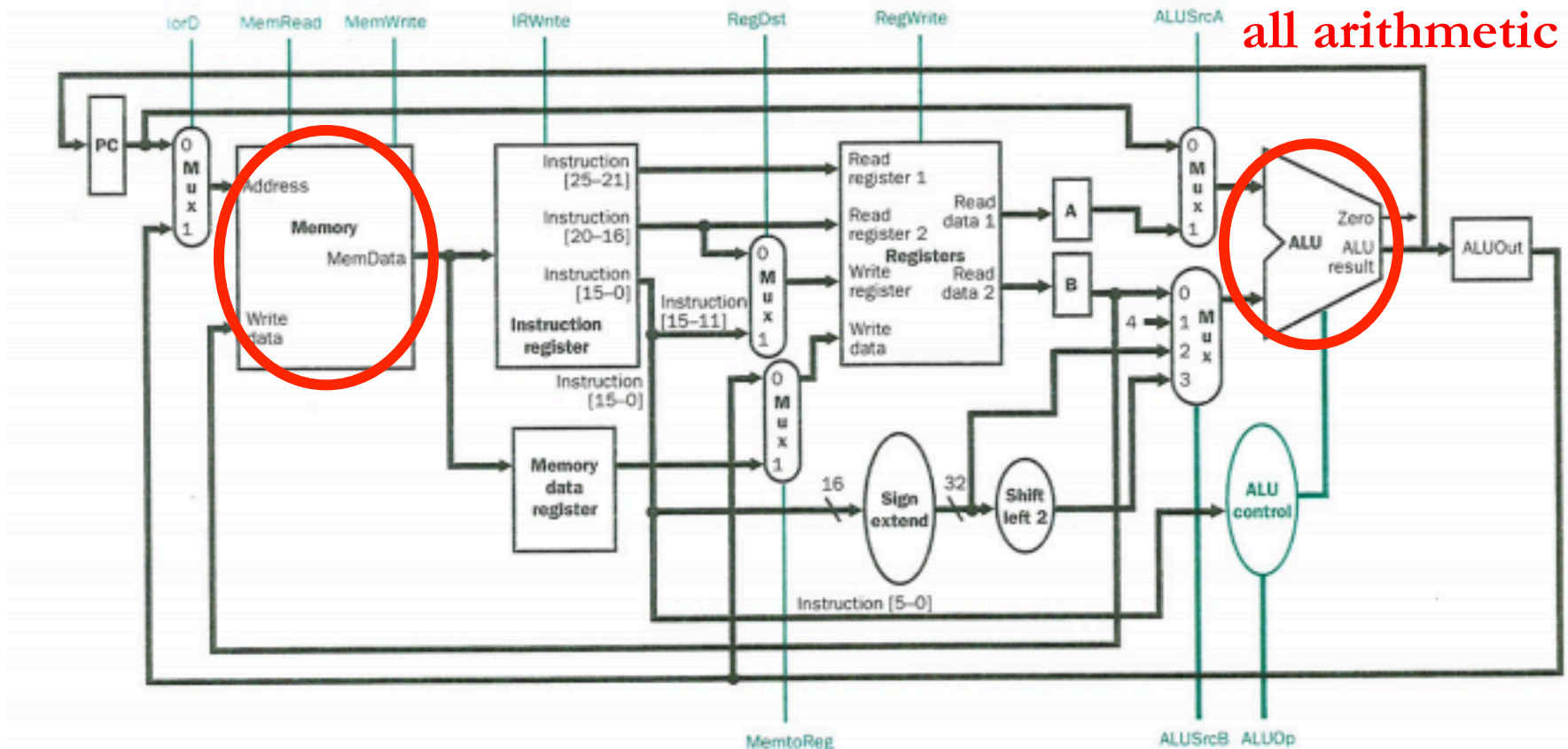


Multi-cycle datapath (overview)

Select address input to
I+D memory

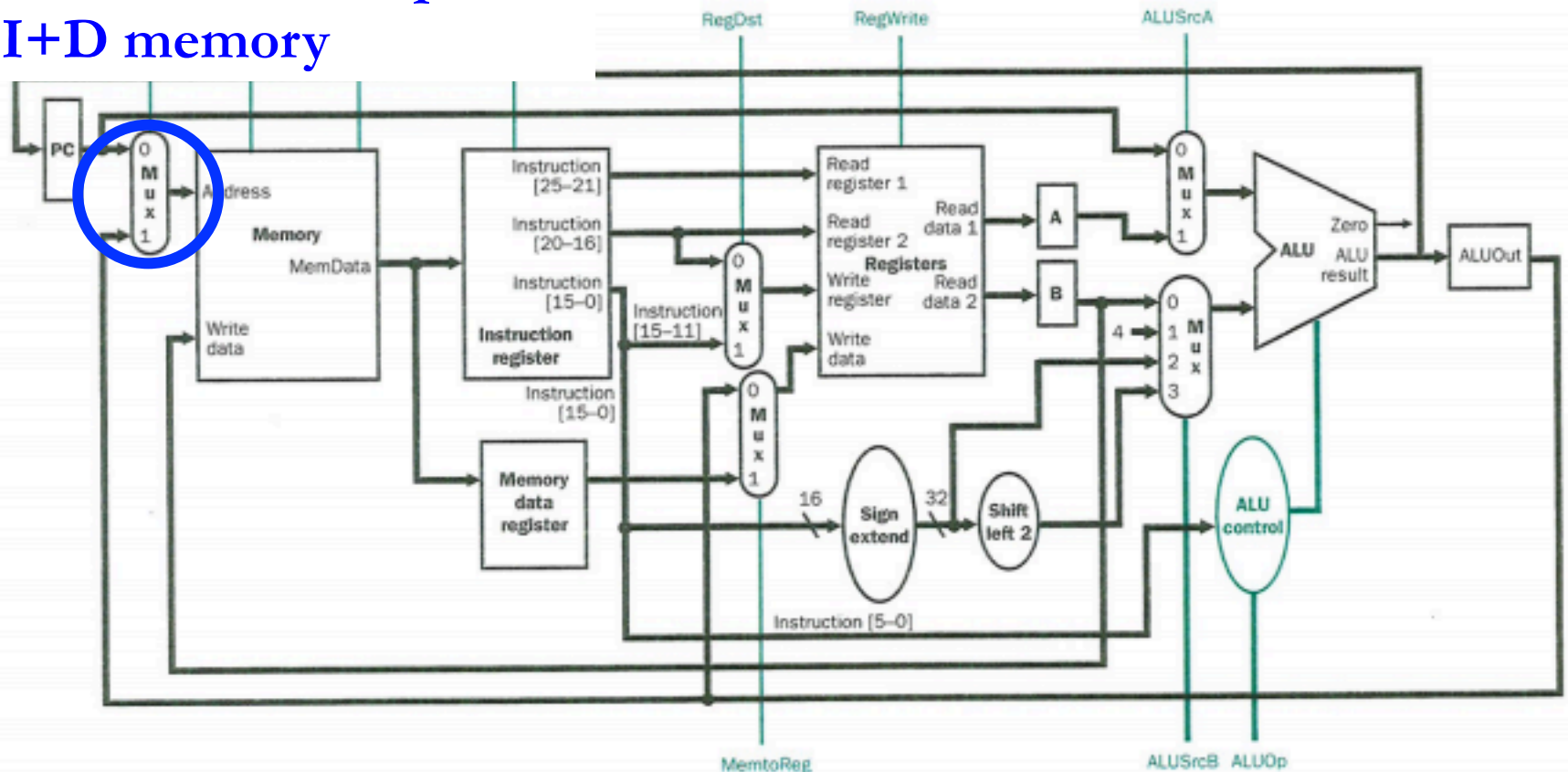


Multi-cycle datapath (overview)

Instruction Register (IR)

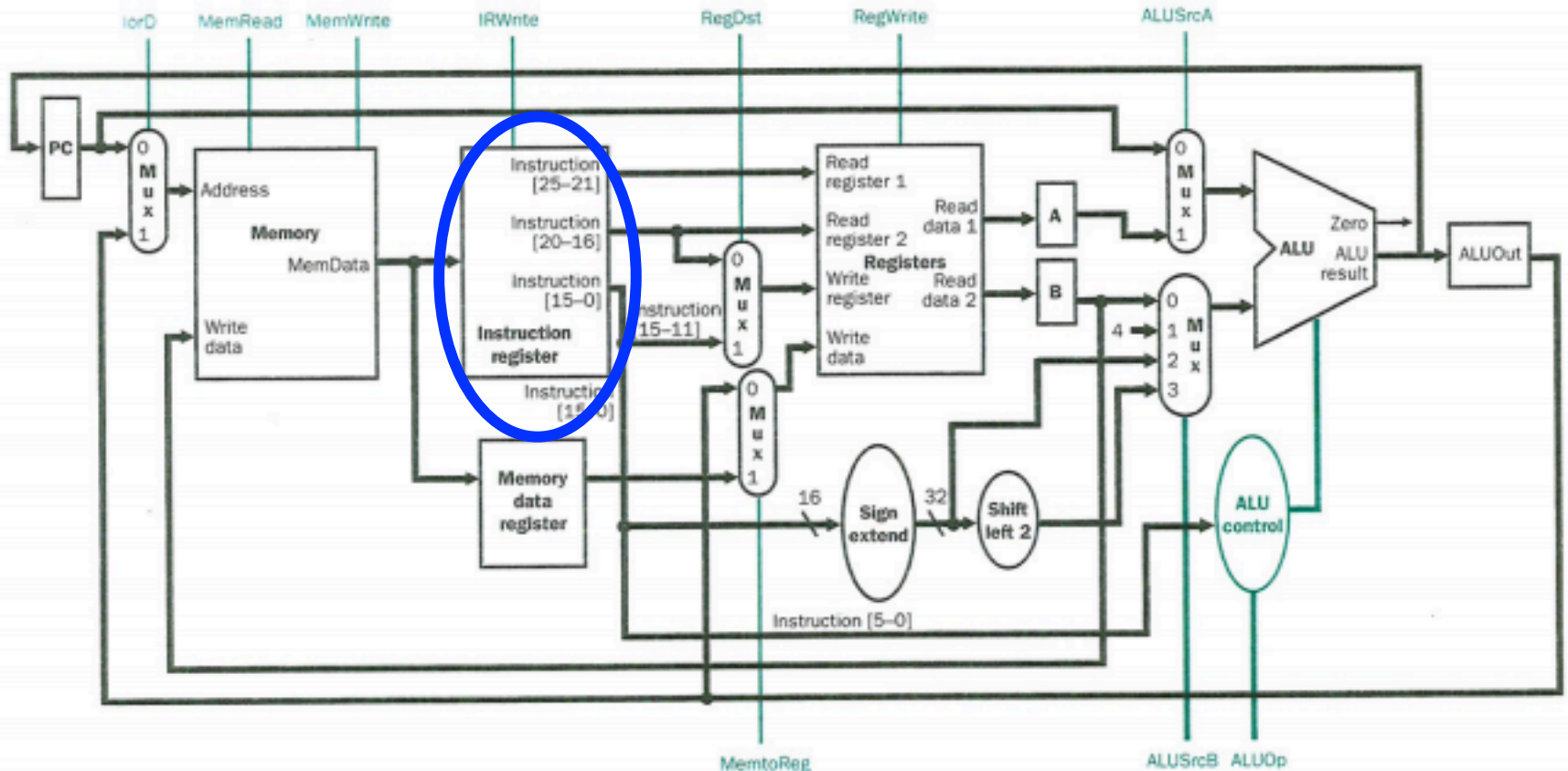


Multi-cycle datapath (overview)

Read Registers A & B

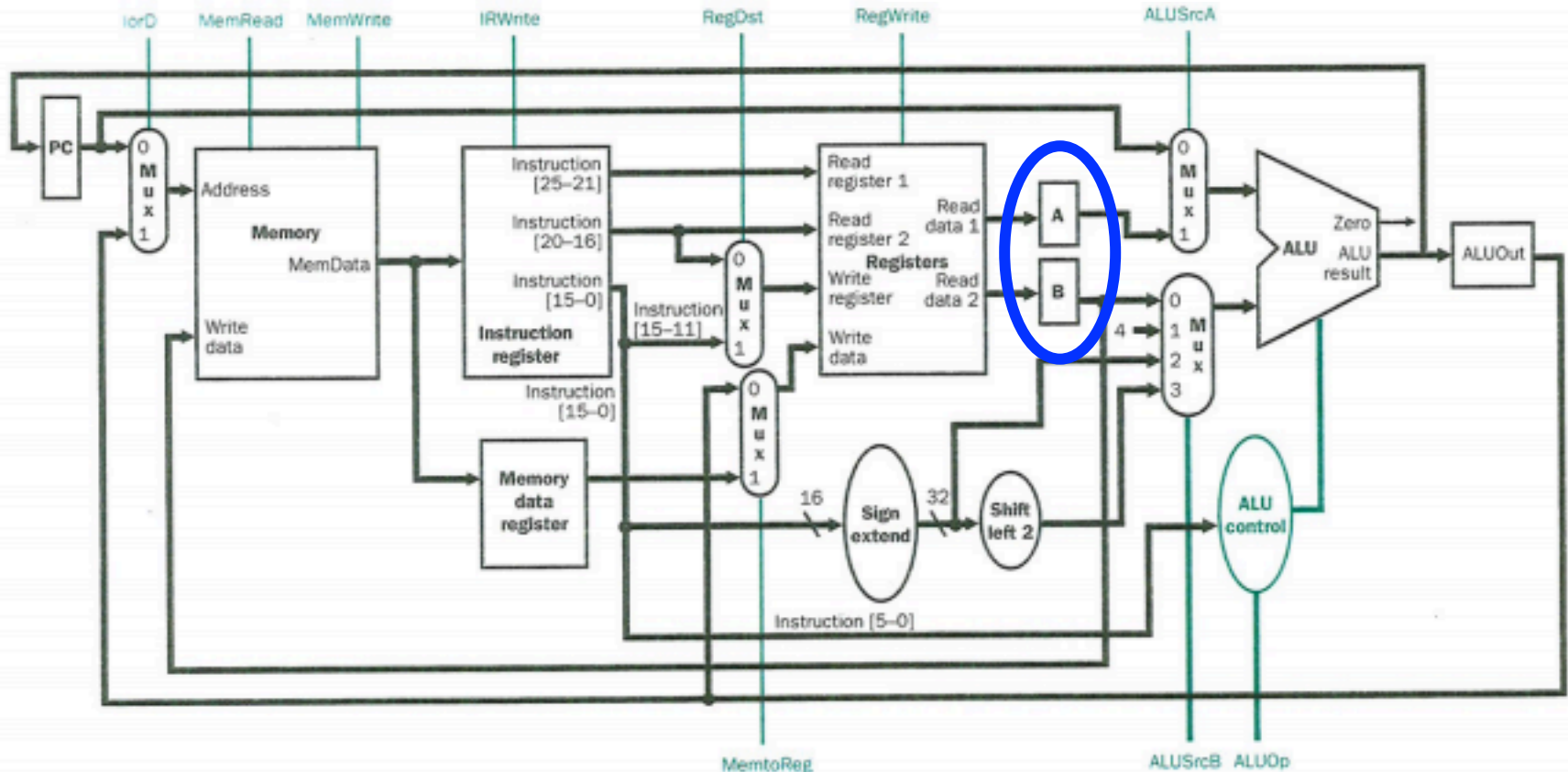

Multi-cycle datapath (overview)

ALU mux 1:
RegA or PC

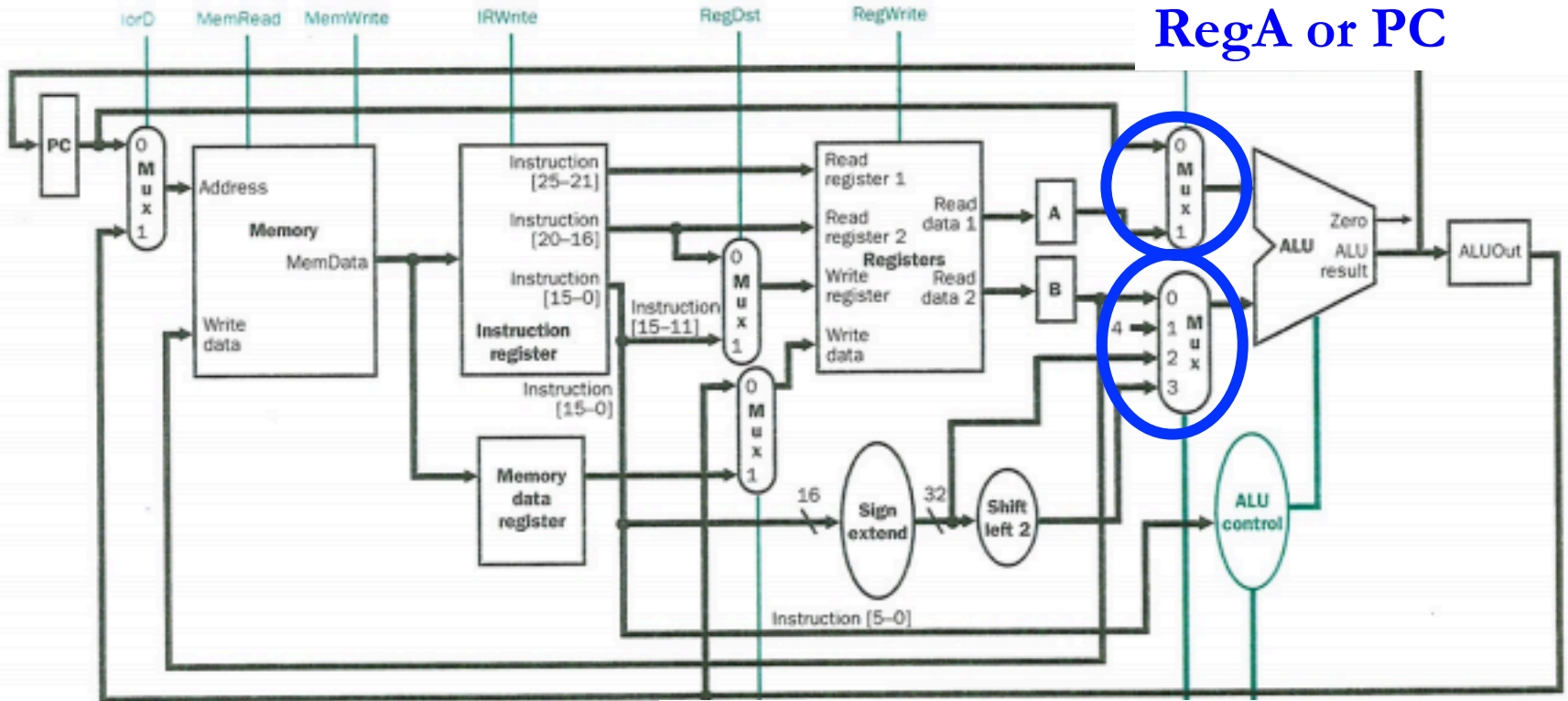


ALU mux 2:

(1) RegB; (2) +4

(3) sign-extended immediate


(4) sign-extended shifted immediate

Multi-cycle datapath (overview)

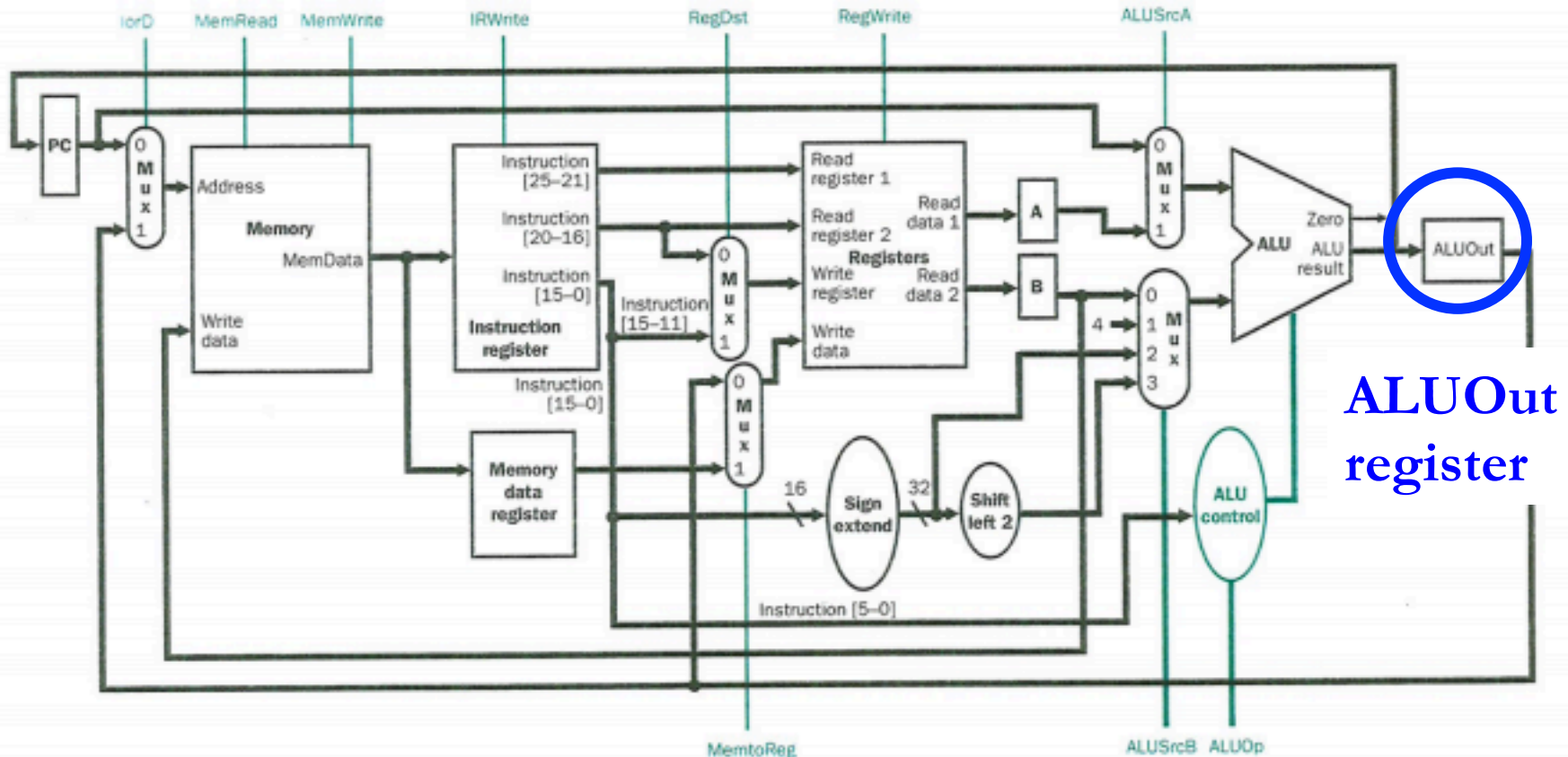


**ALUOut
register**

Multi-cycle datapath (overview)

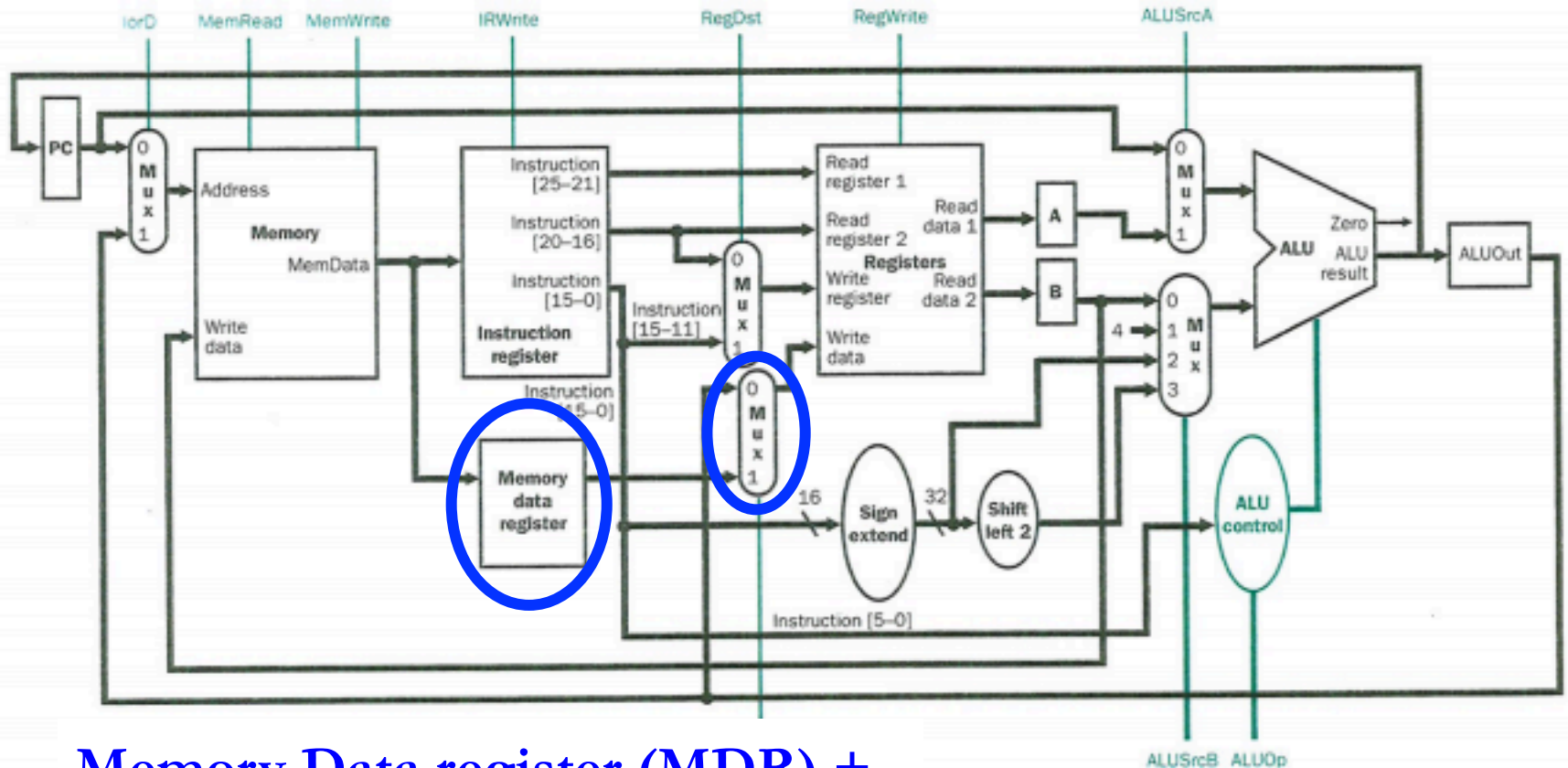

**Memory Data register (MDR) +
Write Data mux**

Multi-cycle datapath (with control)

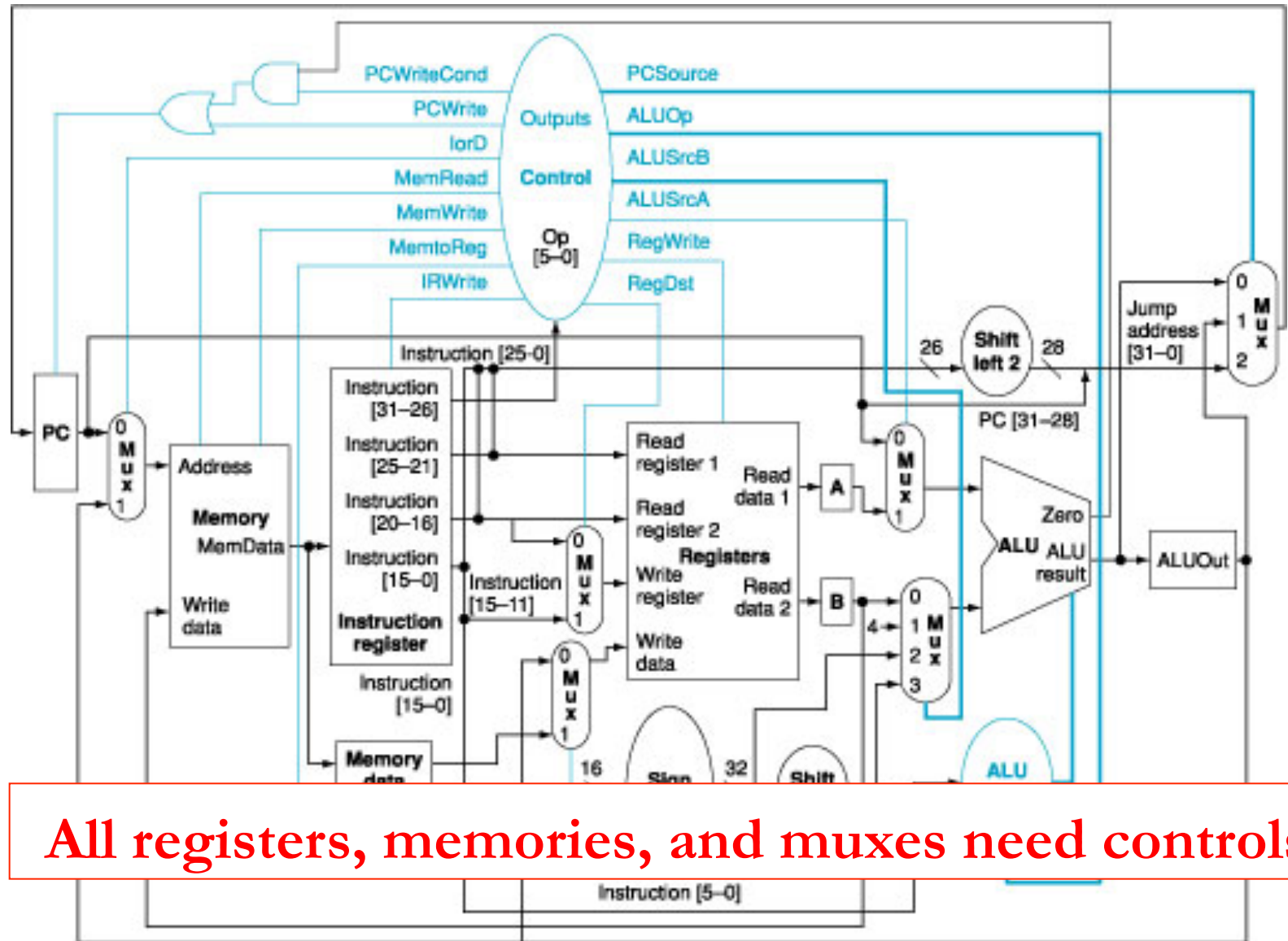

All registers, memories, and muxes need controls

Multi-cycle processor control signals (1-bit)

Signal name	Function
RegDst	Write register in the register file (<i>rs</i> or <i>rd</i>)
RegWrite	Write the register selected via RegDst?
ALUSrcA	Select ALU input A (<i>PC</i> or <i>A</i> register)
MemRead	Read the memory (could be for instruction fetch or data load)
MemWrite	Write the memory
MemtoReg	Select the source of data (data from register or <i>MDR</i>)
IorD	Select the source of the address for the memory unit (<i>PC</i> or <i>ALUout</i>)
IRWrite	Write the IR with output of the memory unit
PCWrite	Write the PC register (source controlled by <i>PCSource</i>)
PCWriteCond	Write the PC if <i>Zero</i> output from the ALU is active

New in multi-cycle processor



Multi-cycle processor control signals (2-bit)


Signal name	Value	Function
ALUSrcB	00	Second ALU input comes from B register
	01	Second ALU input is a constant 4
	10	Second ALU input is sign-extended lower 16 bits of IR
	11	Second ALU input is sign-extended lower 16-bits of IR shifted left by 2
ALUOp	00	ALU performs an Add
	01	ALU performs a Subtract
	10	ALU action determined by FUNCT field
PCSource	00	Output of the ALU (PC+4)
	01	ALUout (branch target address)
	10	Jump target address (IR[25-0] shifted left 2 bits and combined with PC+4[31-28])



How to design the control

- The control unit of a multicycle processor is an FSM
- For a given instruction type, determines the sequence of control signals on a cycle-by-cycle basis
 - On a given cycle: outputs the control signals and next FSM state

Control FSM overview

 

- Fetch & Decode common for all insts
 - 2 cycles (Fetch, Decode)
- Rest: depends on the inst type
 - 1 to 3 additional cycles

What happens in each cycle – 1 & 2

1. Instruction fetch

$IR \leq Mem[PC]$

$PC \leq PC + 4$


2. Instruction decode and register fetch

$A \leq Reg[IR[25:21]]$

$B \leq Reg[IR[20:16]]$

$ALUOut \leq PC + sgnext(IR[15:0] \ll 2)$

Cycle 2 –instr decode & reg read (all)

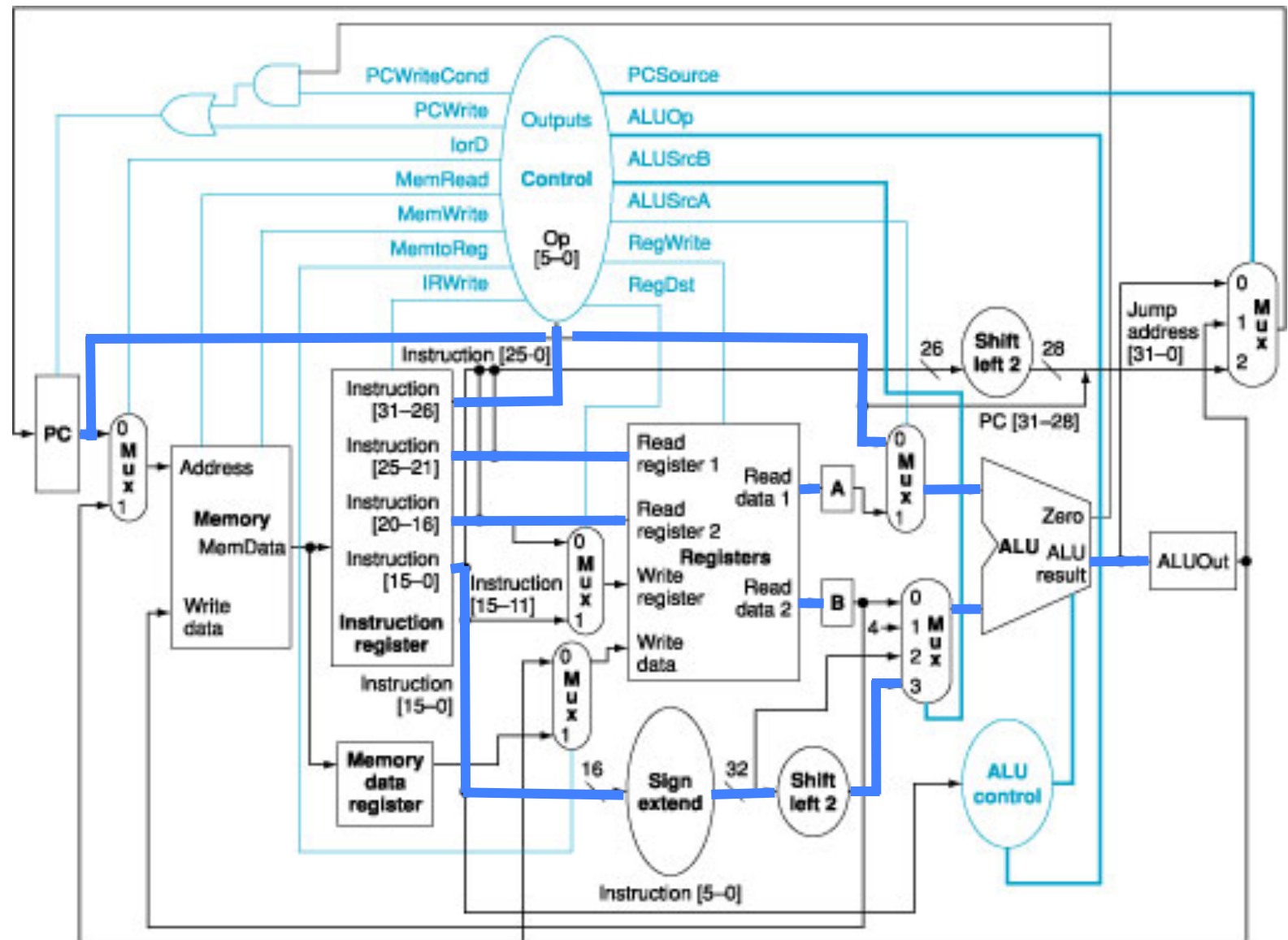

What happens in each cycle – 3

3a. Memory address generation

$\text{ALUOut} \leq A + \text{sgnnext}(\text{IR}[15:0])$

3b. R-type arithmetic-logical instruction

$\text{ALUOut} \leq A \text{ op } B$

3c. Branch completion


$\text{if } (A == B) \text{ PC} \leq \text{ALUOut}$

3d. Jump completion


$\text{PC} \leq \{ \text{PC}[31:28], \text{IR}[25:0], 2'b00 \}$




Cycle 3a: add imm arg (addi, lw, sw)

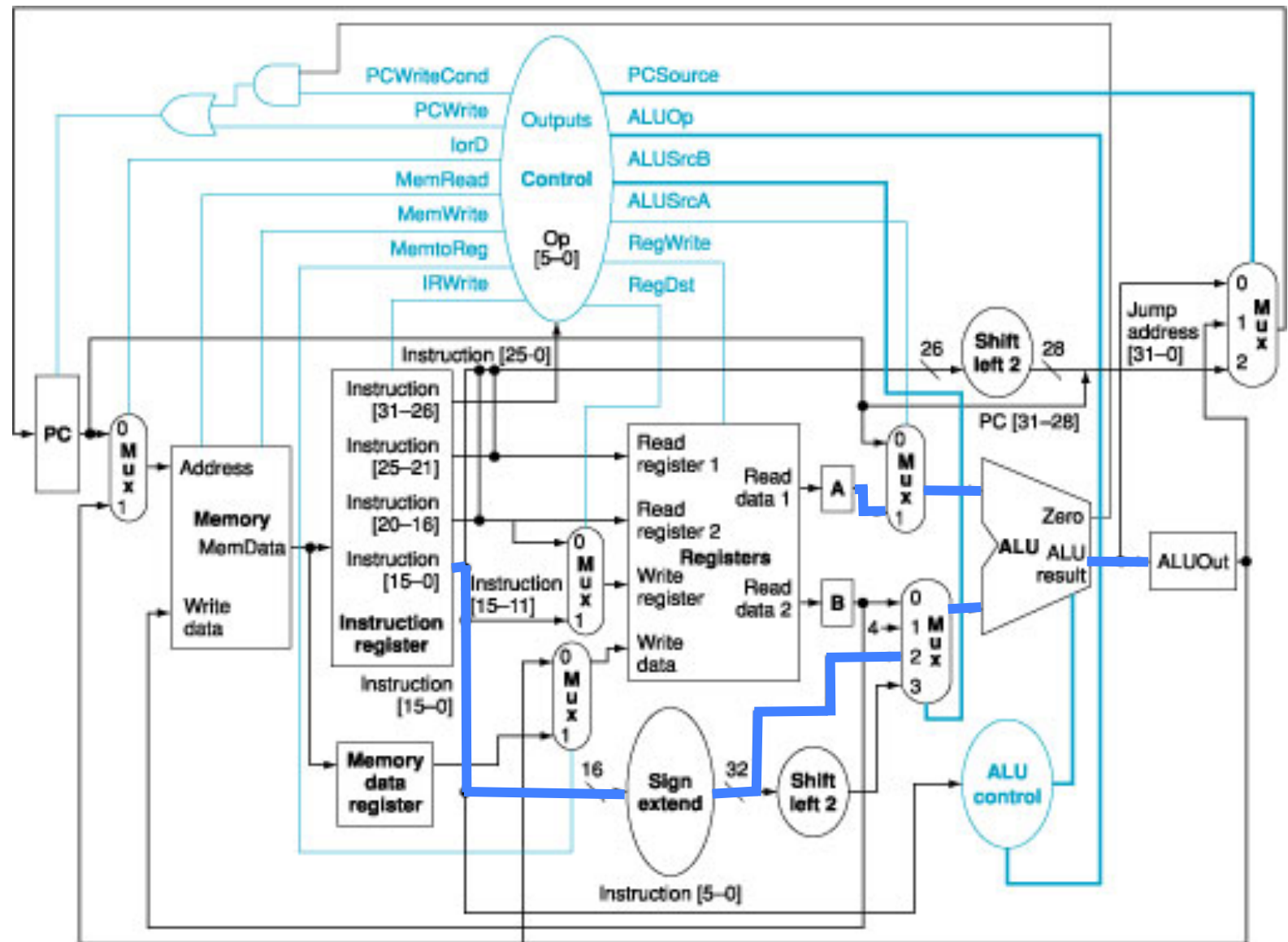


Cycle 3b: R-type ALU op (add, and)

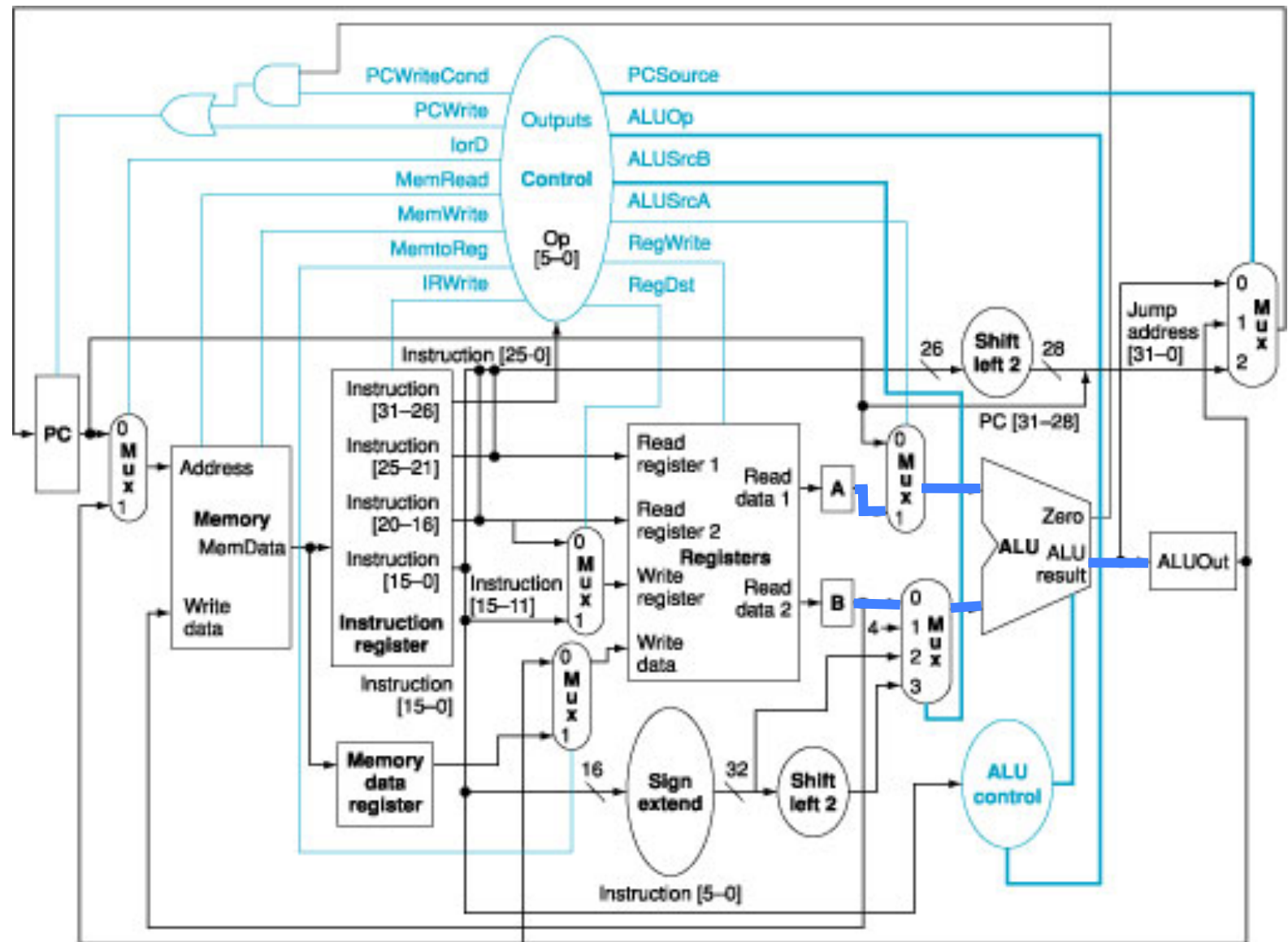

Cycle 3c: Branch taken (beq, bne)

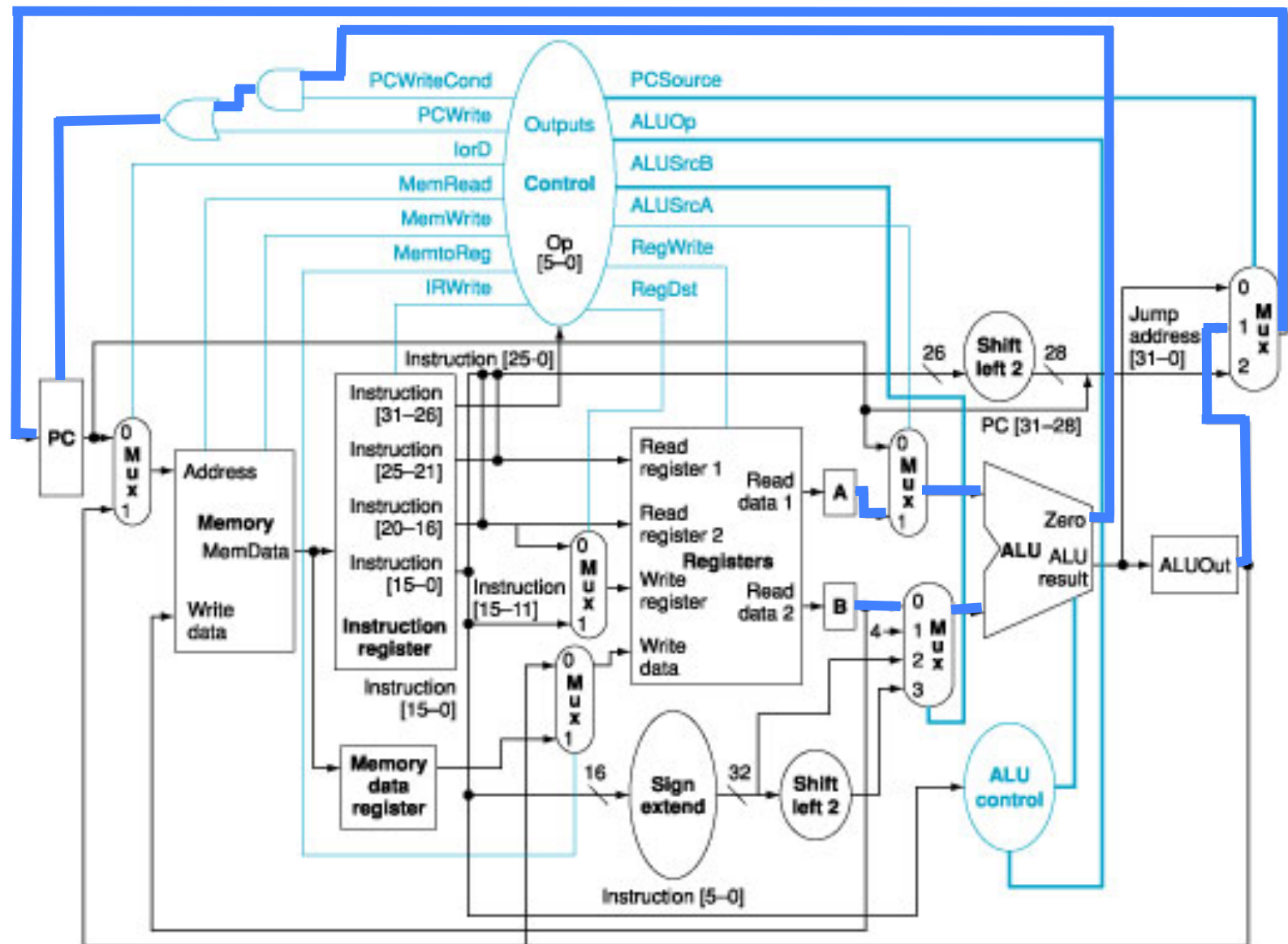

Cycle 3d: jump (j)

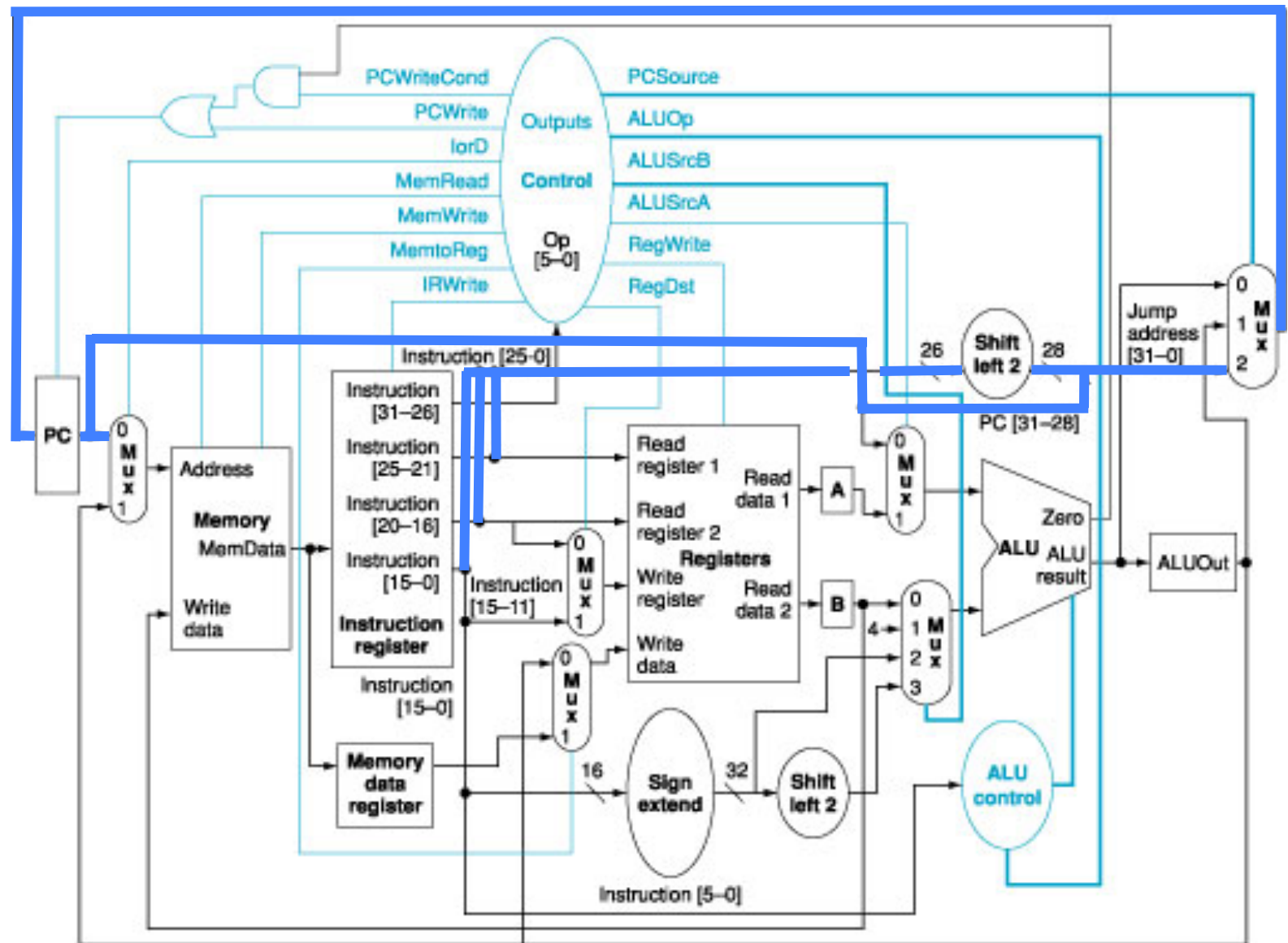

What happens in each cycle – 4

4a. R-type arith-logical instruction completion

$\text{Reg}[\text{IR}[15:11]] = \text{ALUOut}$


4b. Memory access (load)

$\text{MDR} \leq \text{Mem}[\text{ALUOut}]$


4c. Memory access (store) & completion

$\text{Mem}[\text{ALUOut}] \leq B$


Cycle 4a: R-type result write (add, and)

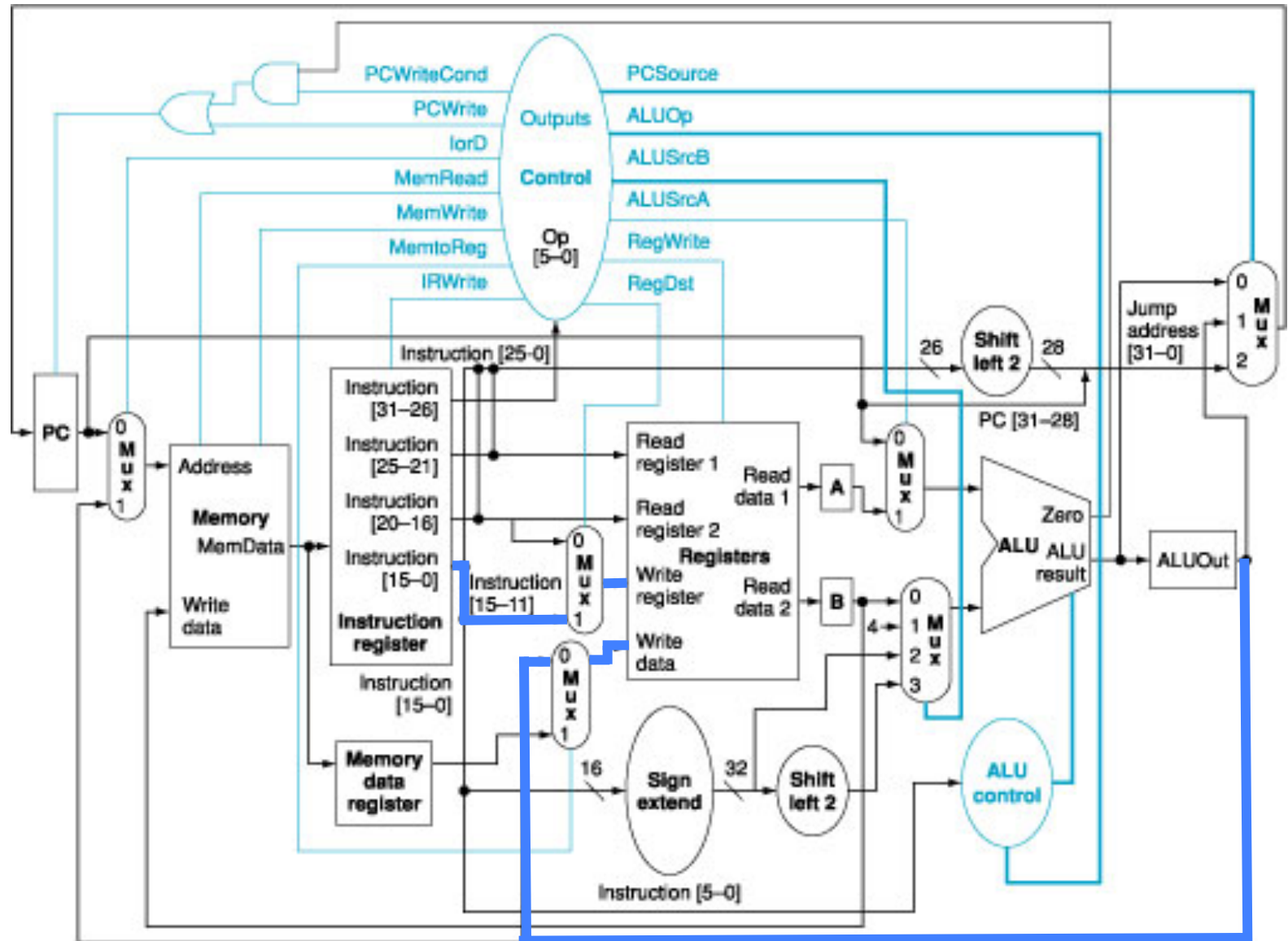

Cycle 4b: Load from mem (lw)

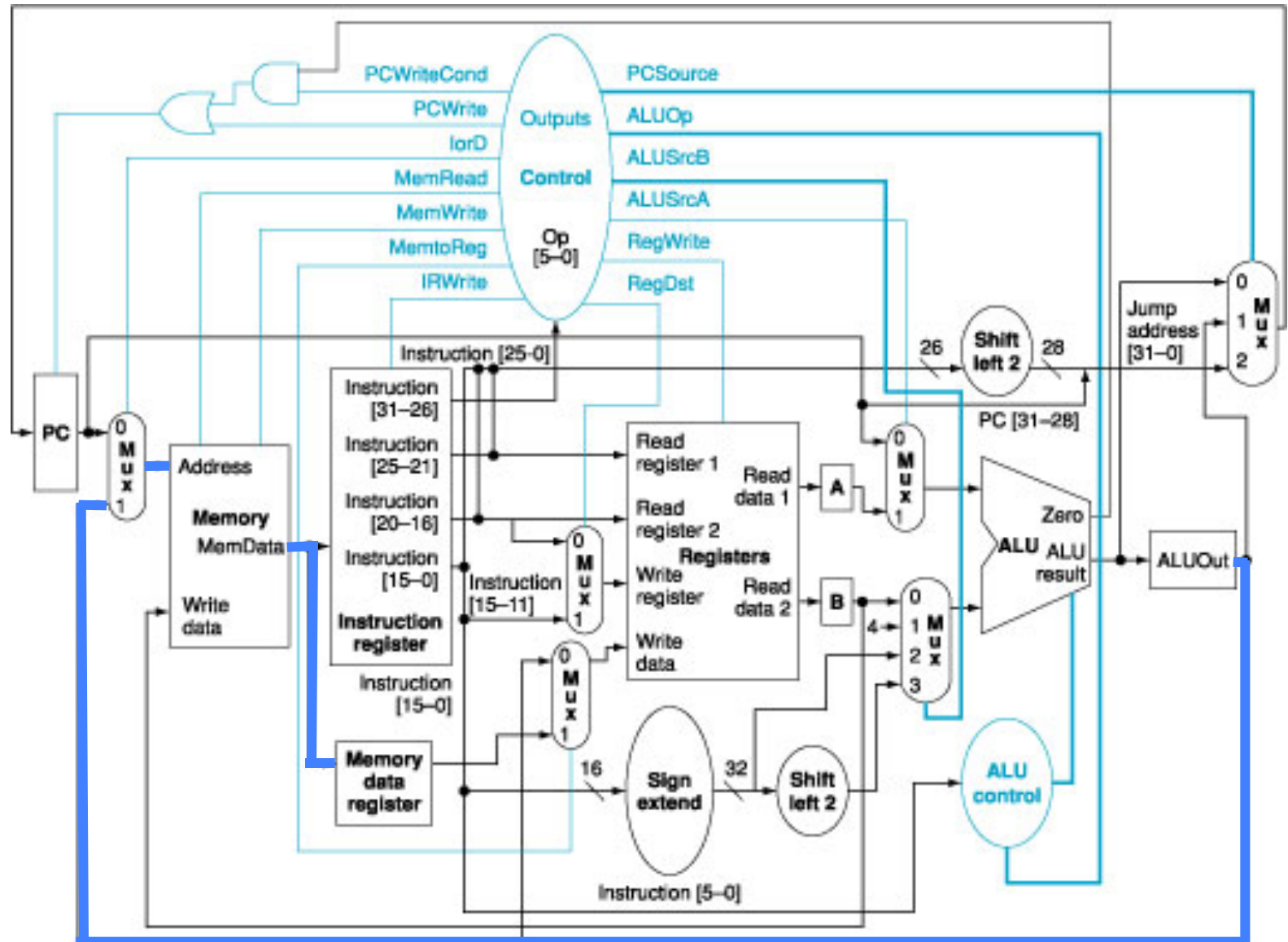

Cycle 4c: Store to mem (sw)

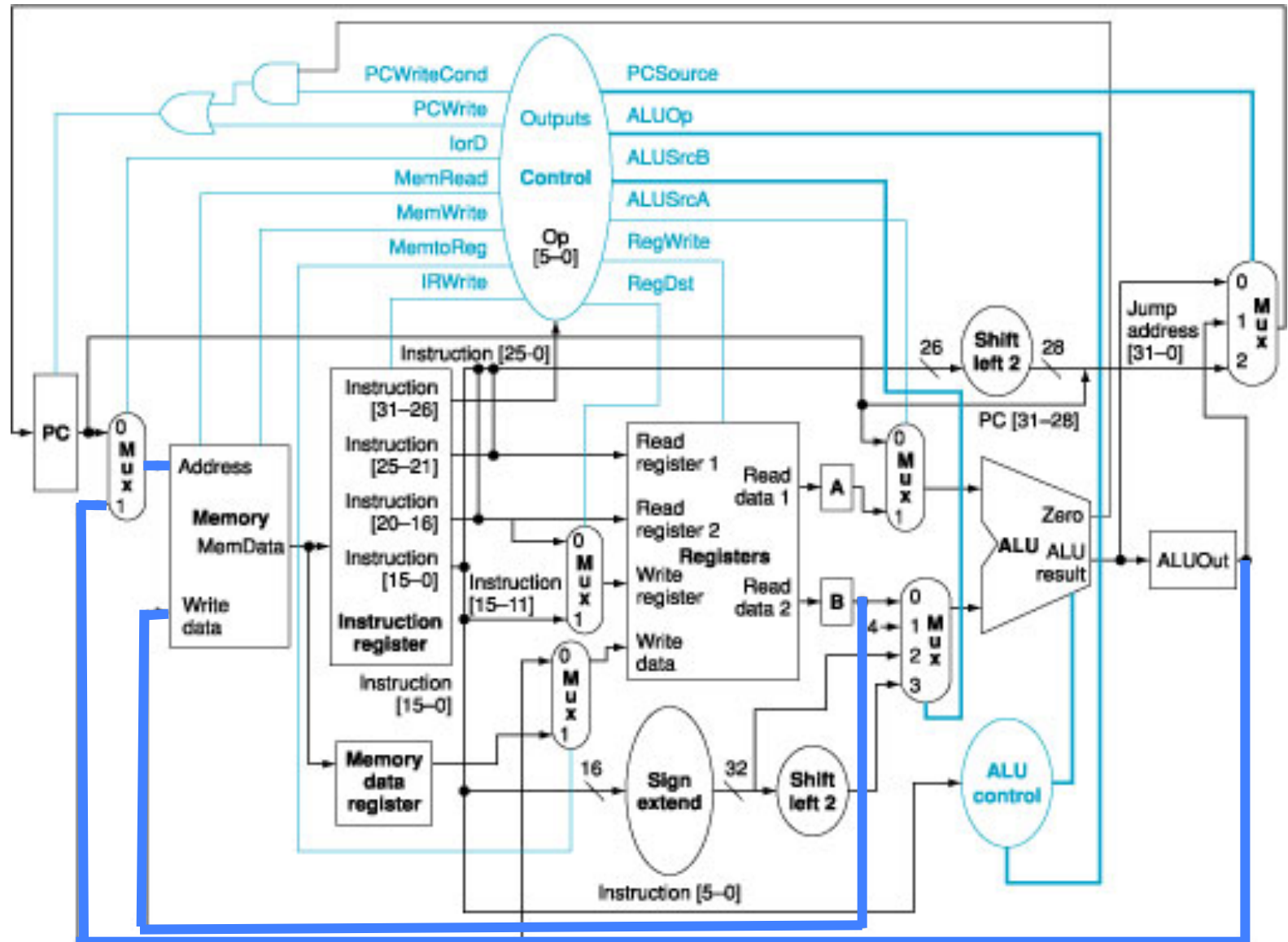


What happens in each cycle – 5


5. Load instruction completion

$\text{Reg}[\text{IR}[20:16]] \leq \text{MDR}$

Cycle 5: save of loaded value (lw)

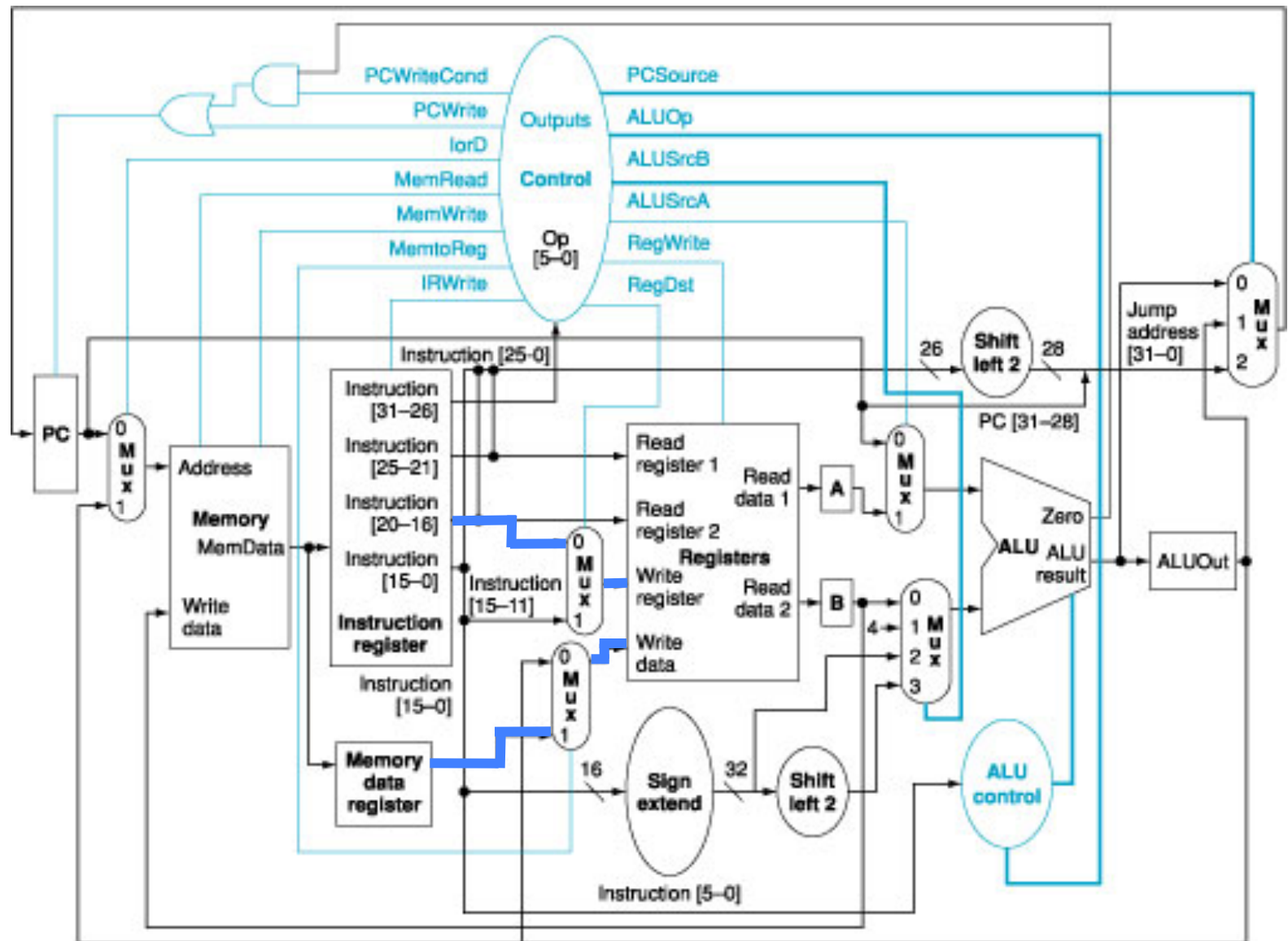


Designing the Control Unit

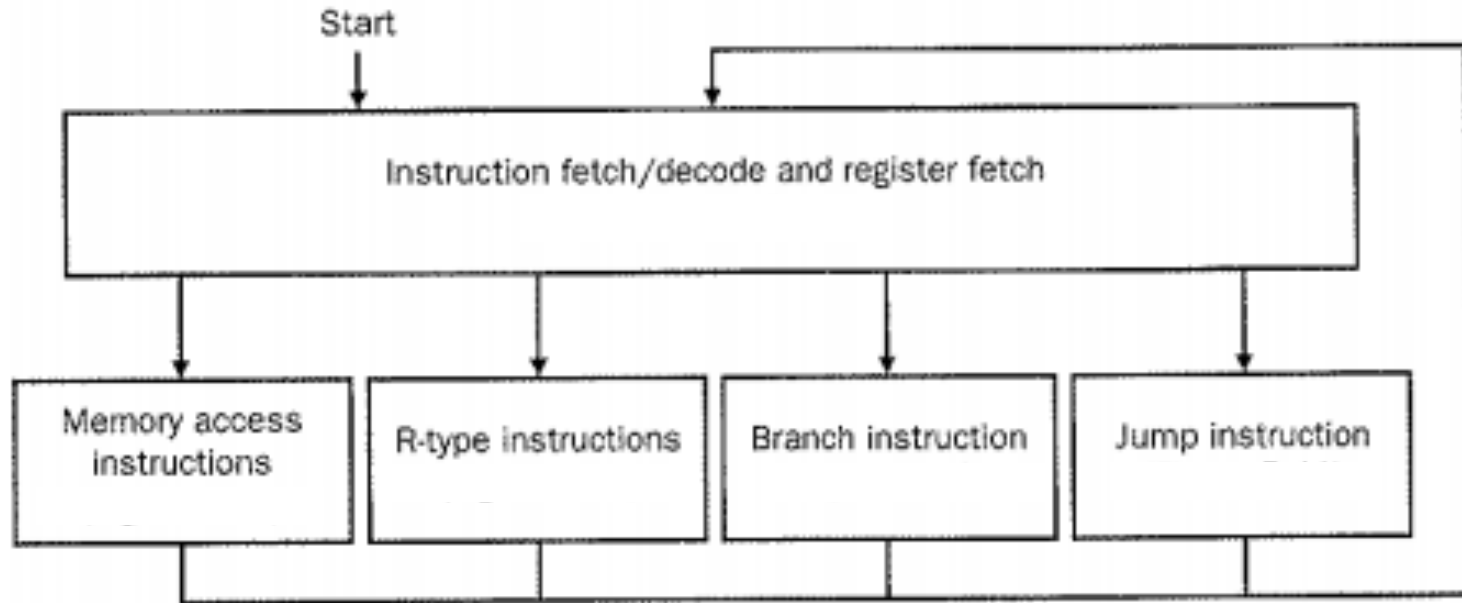


- Fetch & Decode common for all insts
 - 2 cycles total (Fetch, Decode)
- Rest: depends on the inst type
 - 1 to 3 additional cycles


Fetch and Decode States

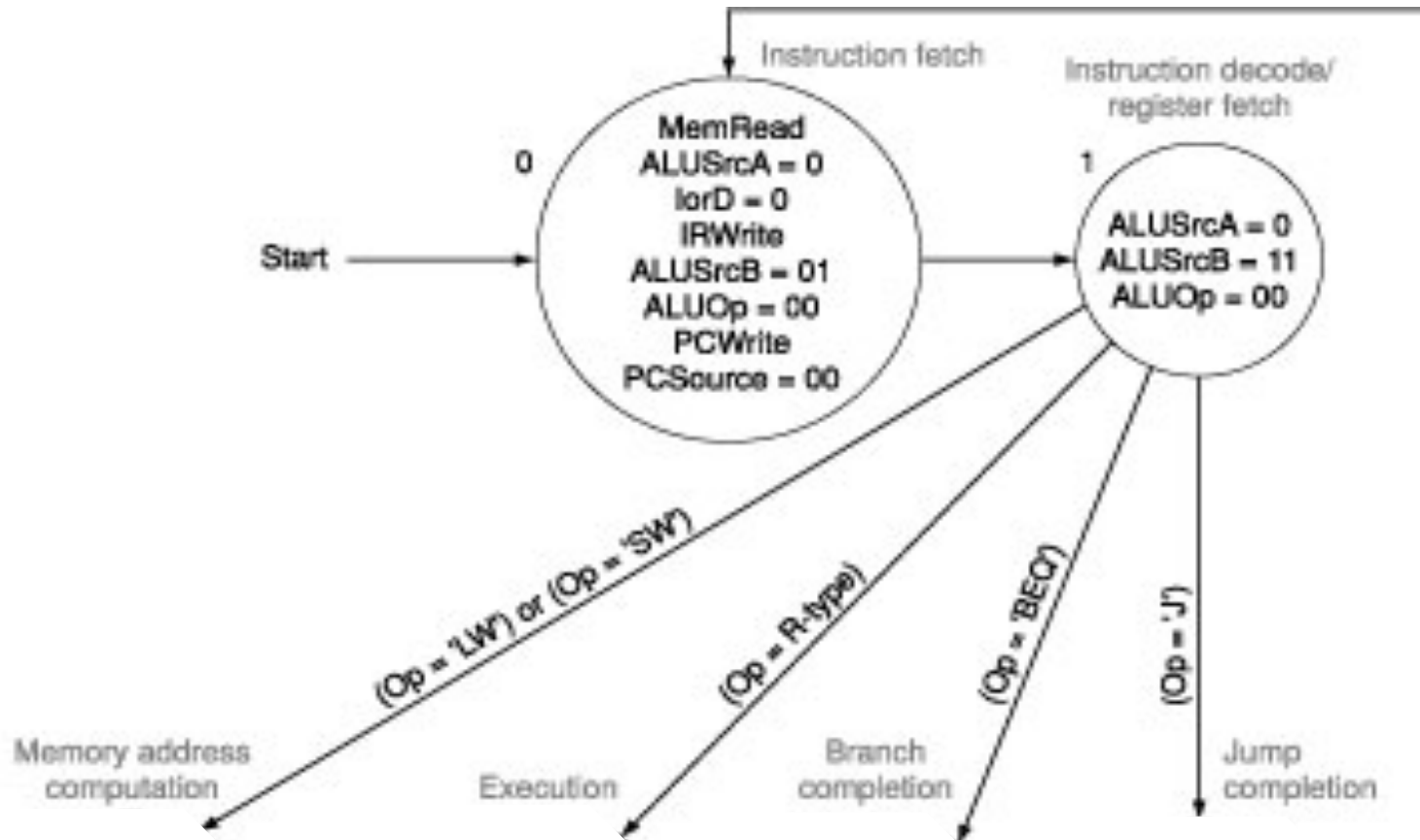

Memory Access States

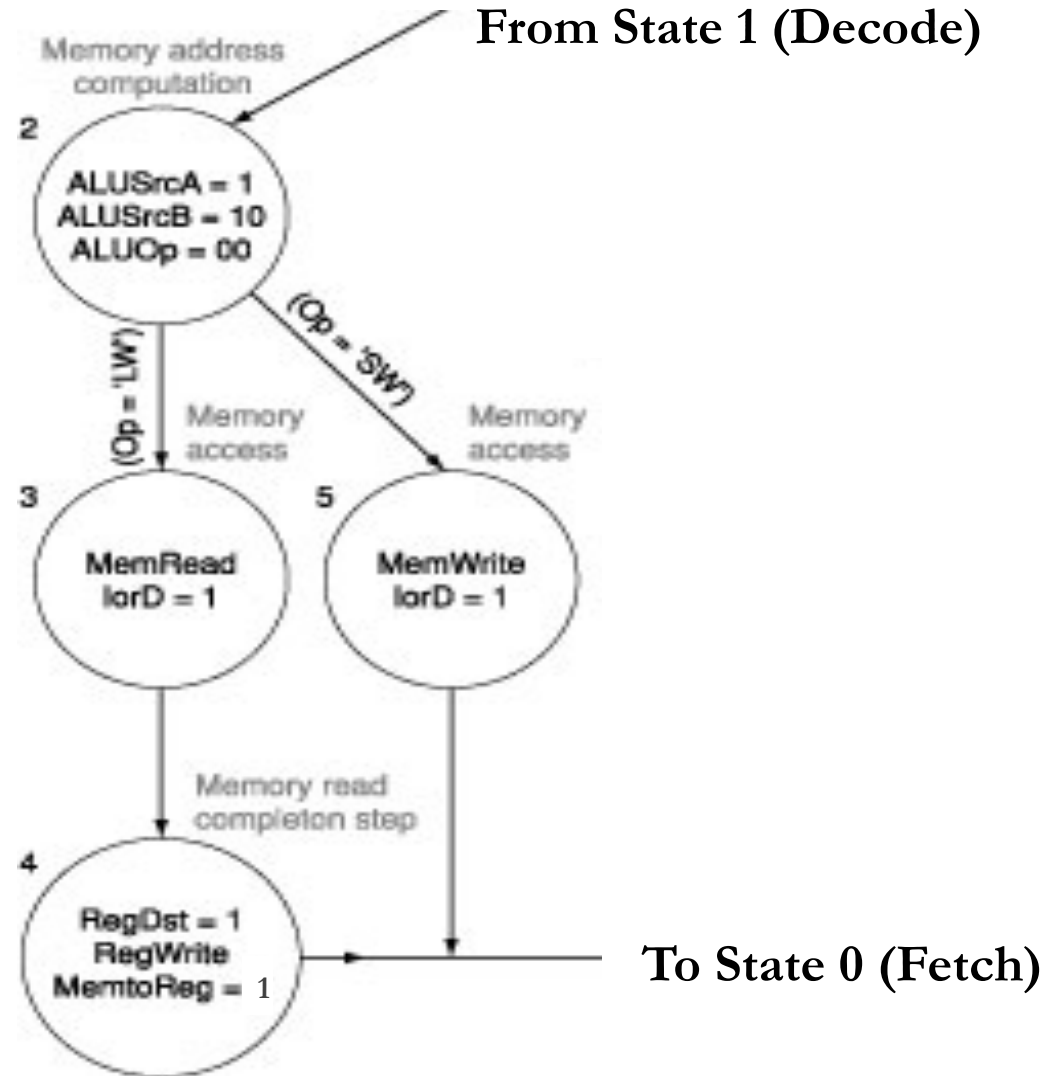


R-Type Instruction States

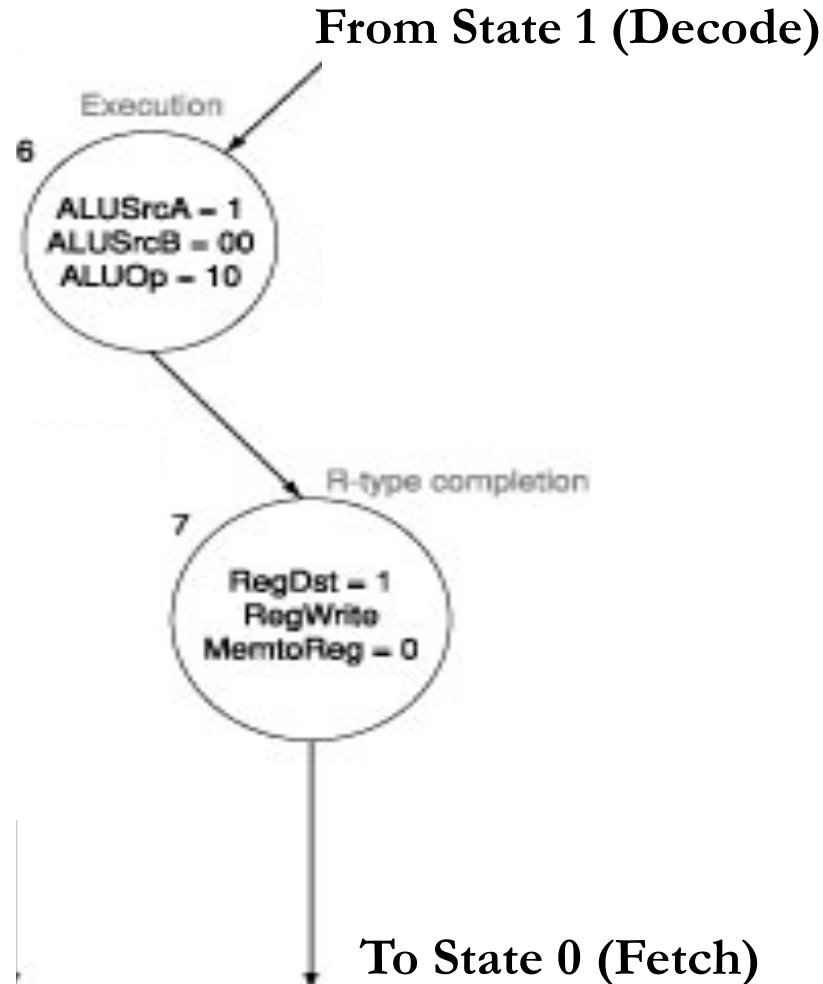


Branch Resolution States


From State 1 (Decode)

 

Jump Resolution States

From State 1 (Decode)

 

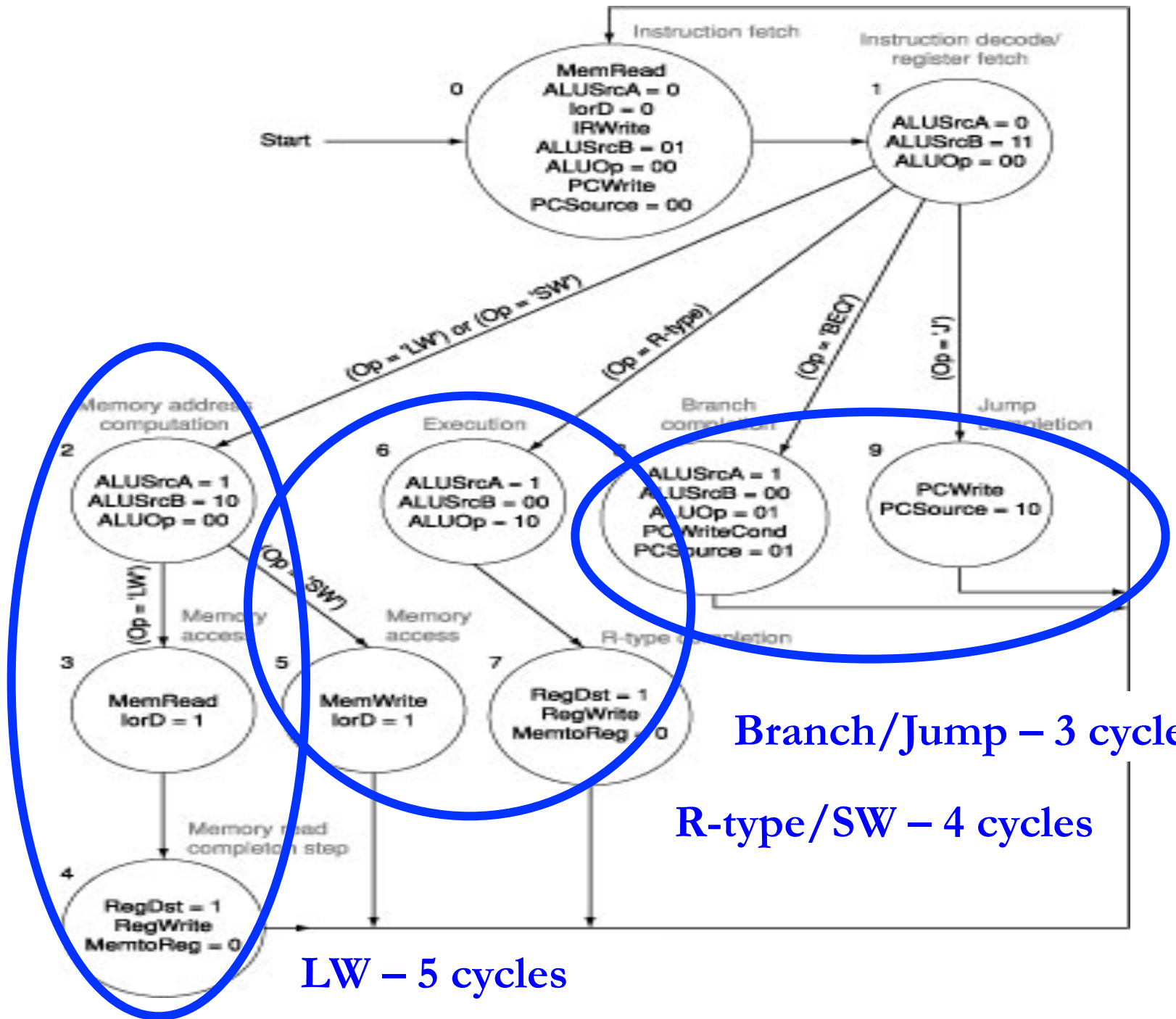

Implications of Processor Design Choices

Execution time =

$$\begin{array}{c} \text{instruction count} \\ \times \\ \text{cycles per instruction} \\ \times \\ \text{cycle time} \end{array}$$

**Single- vs multi-cycle processor:
which one should yield higher performance?**

