

Inf2C - Computer Systems

Lecture 10-11

Processor Design – Single Cycle

Boris Grot

School of Informatics
University of Edinburgh




Previous lectures

- Combinational circuits
 - Combinations of gates (INV, AND, OR, NOR..)
 - Output: function of the input only (memory-less)
- Sequential circuits
 - Output: function of the input and prev inputs
 - Basic memory element: SR-latch (cross-coupled NORs)
 - Clock: synchronizes the operation of the circuit
 - Operation: current states + inputs go through combinational logic. Next states stored in a register on a rising clock edge.
- Hardware Finite State Machines (FSMs)
 - Registers for states + comb'l logic for transitions & outputs

Lecture 9: Processor design – single cycle

 - Motivation:
 - Learn how to design a simple processor
- Two main parts:
 - Datapath: performs the data operations as commanded by the program instructions
 - Control: controls the datapath, memory and I/O according to the program instructions
- Using:
 - Combinational and sequential circuits described in previous lectures




Design steps / Lecture outline

- Step 1: Determine the components required by understanding main processor functions
- Step 2: Build the datapath
- Step 3: Build the control
- Show the execution of a few instructions on the designed machine

Main processor functions

- **Fetch** instruction from **instruction memory**
- Read the **register** operands
- Use the **ALU** for computation
 - Arithmetic, memory address, branch target address
- Access **data memory** for load/store
- Store the result of computation or loaded data into the destination **register**
- Update the **Program Counter (PC)**


Instruction Fetch: common to all insts

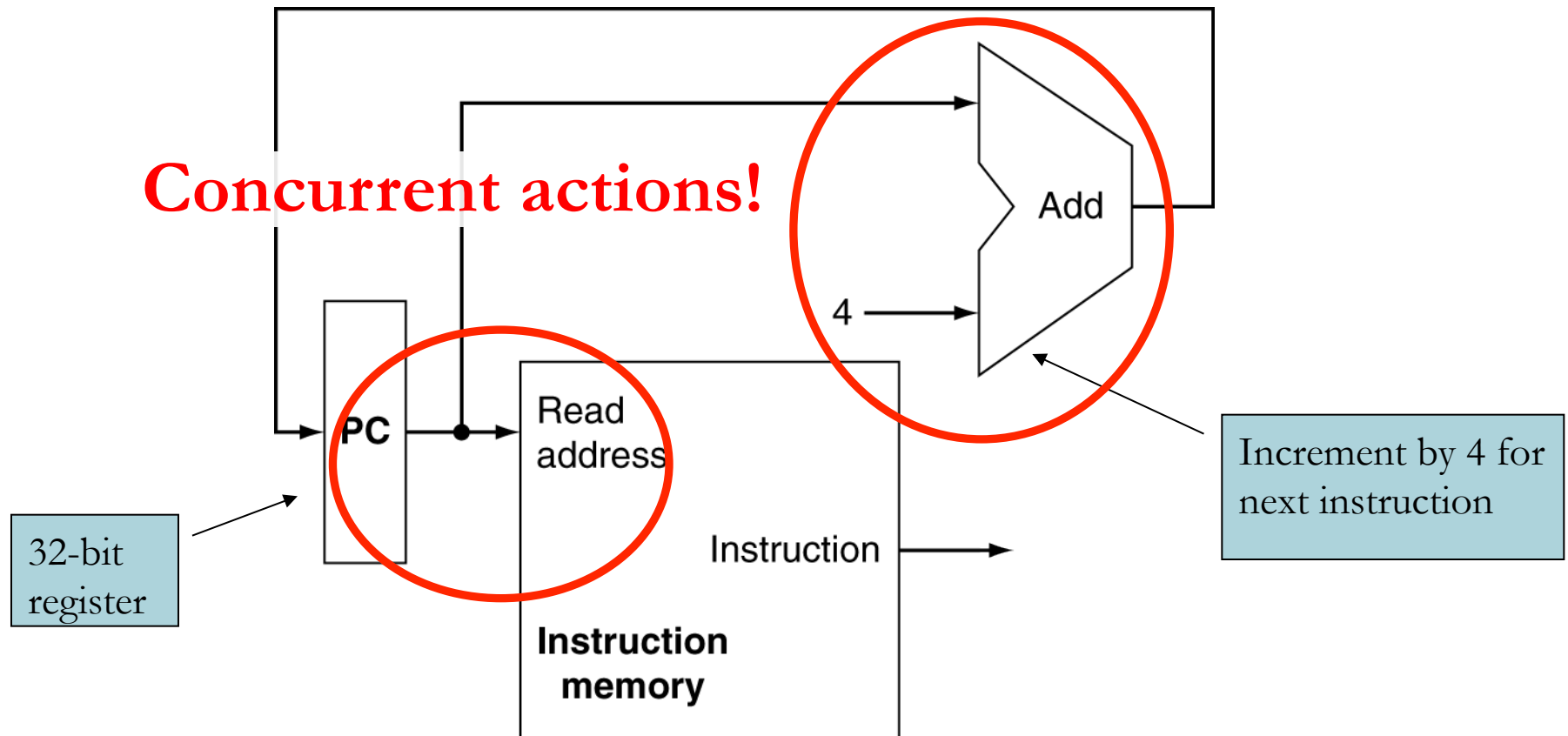

R-Format Instructions


1. Read two register operands
2. Perform arithmetic/logical operation
3. Write register result

A bundle of N wires (N=5 here)

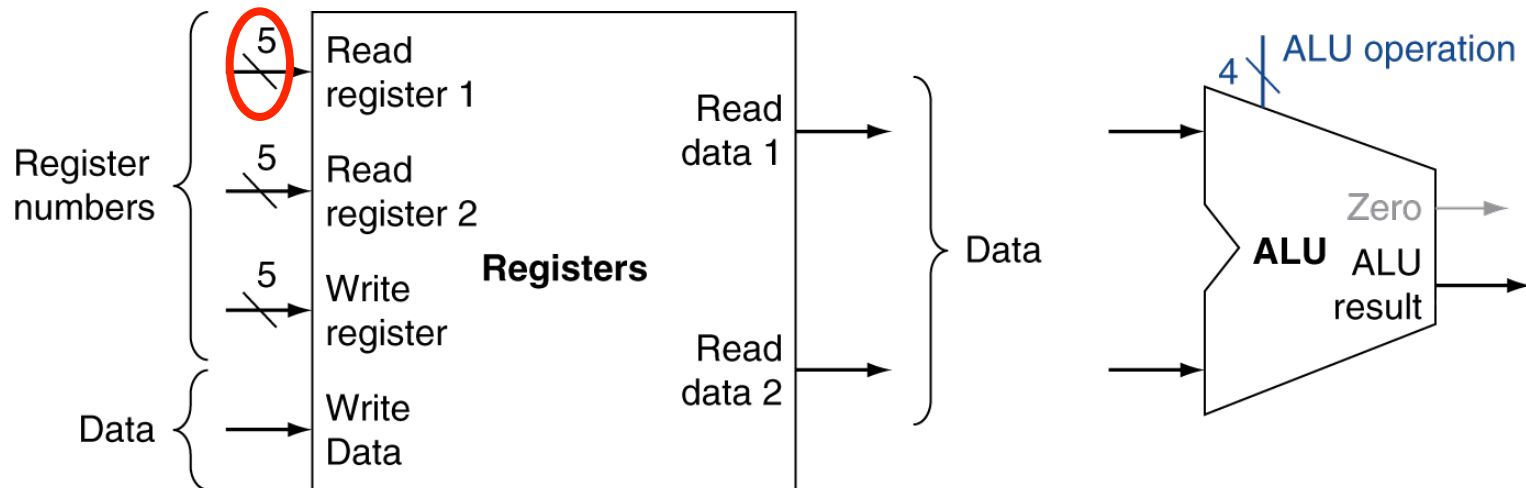

Load/Store Instructions

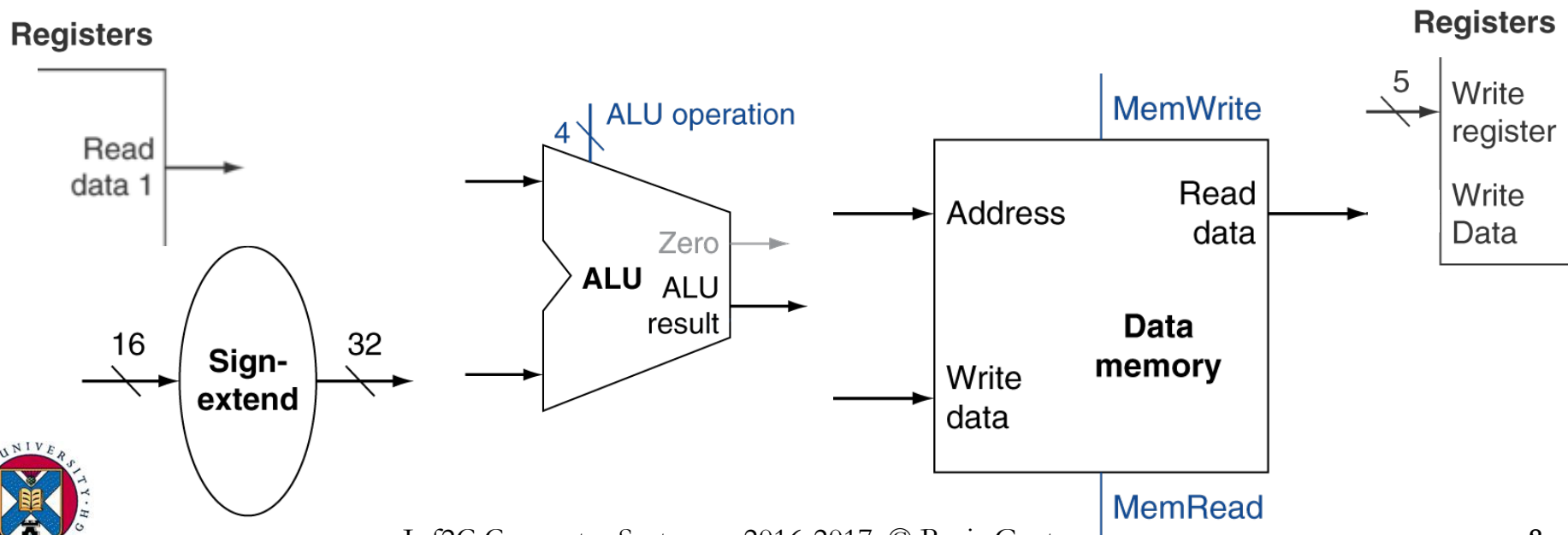
1. Read register operands
2. Calculate address using 16-bit offset
 - Use ALU, but sign-extend offset
3. Read (for load) or write (for store) the memory
4. Load only: update destination register




Branch Instructions

1. Read register operands
2. Compare operands
 - Use ALU, subtract and check Zero output
3. Calculate target address
 - Sign-extend the immediate (offset)
 - Shift left 2 places (word align)
 - Add to PC + 4
 - Already calculated by instruction fetch


Branch Instructions

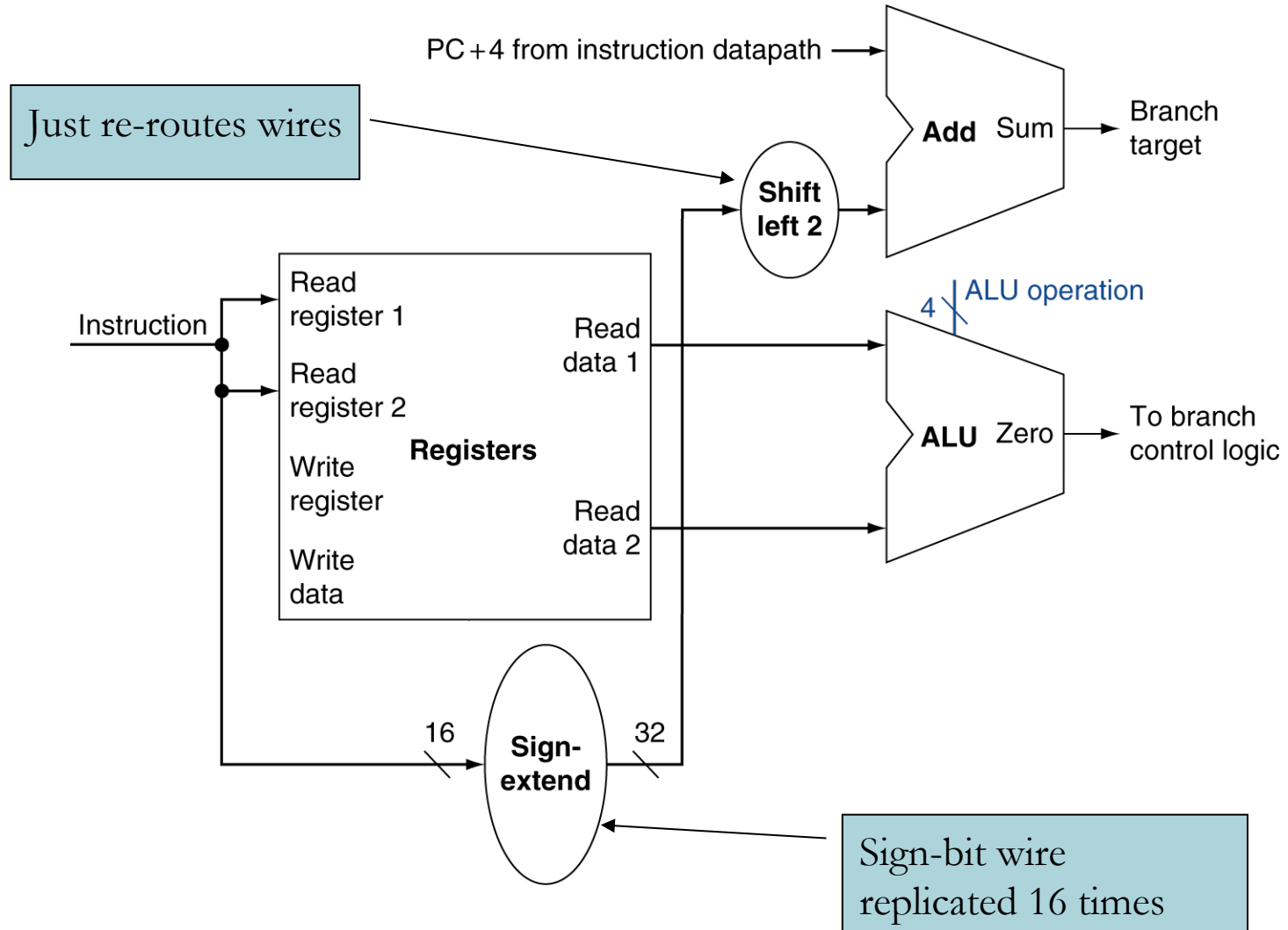


Putting It Together: Simplified Datapath

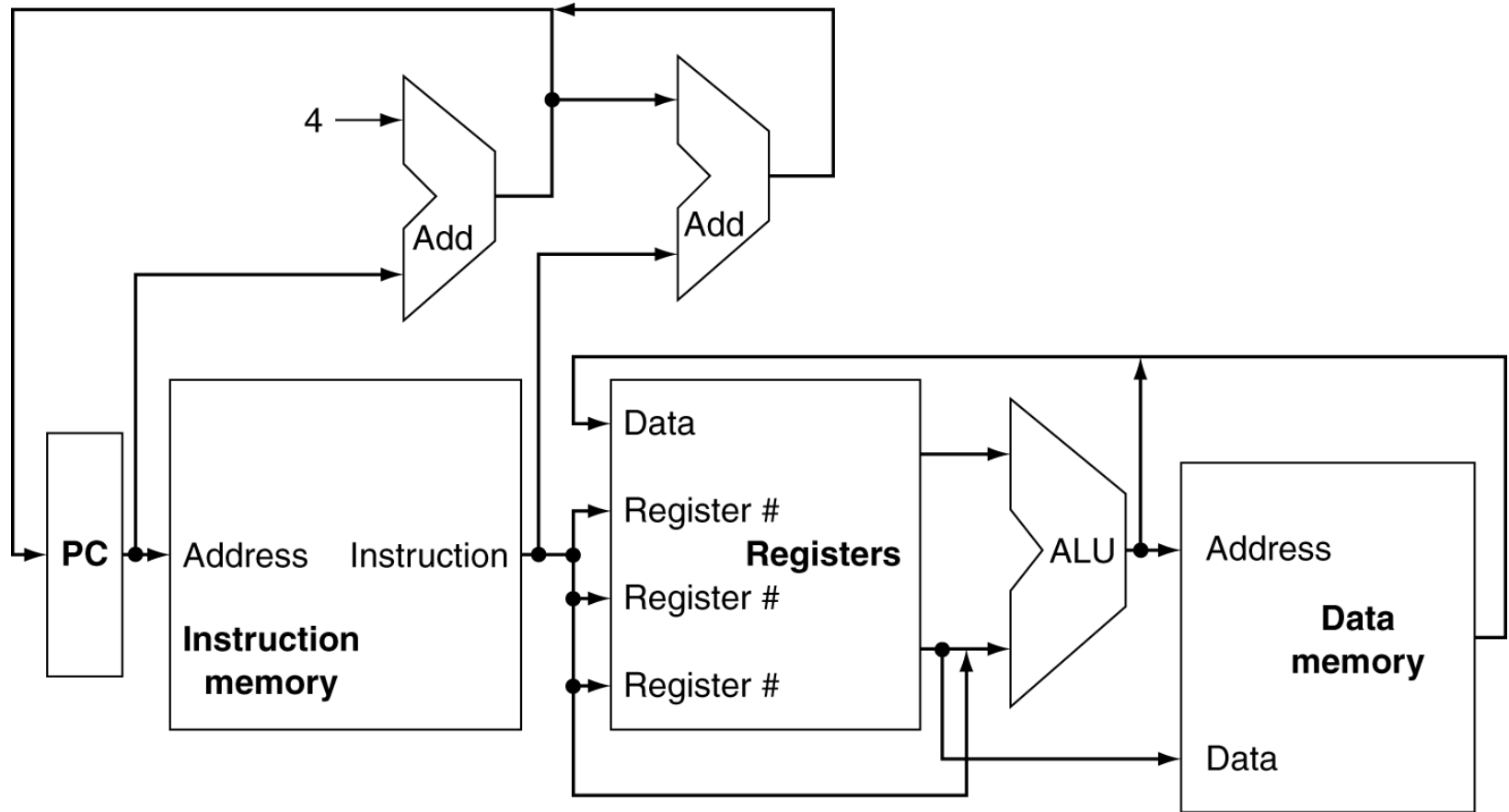


Simplified Datapath

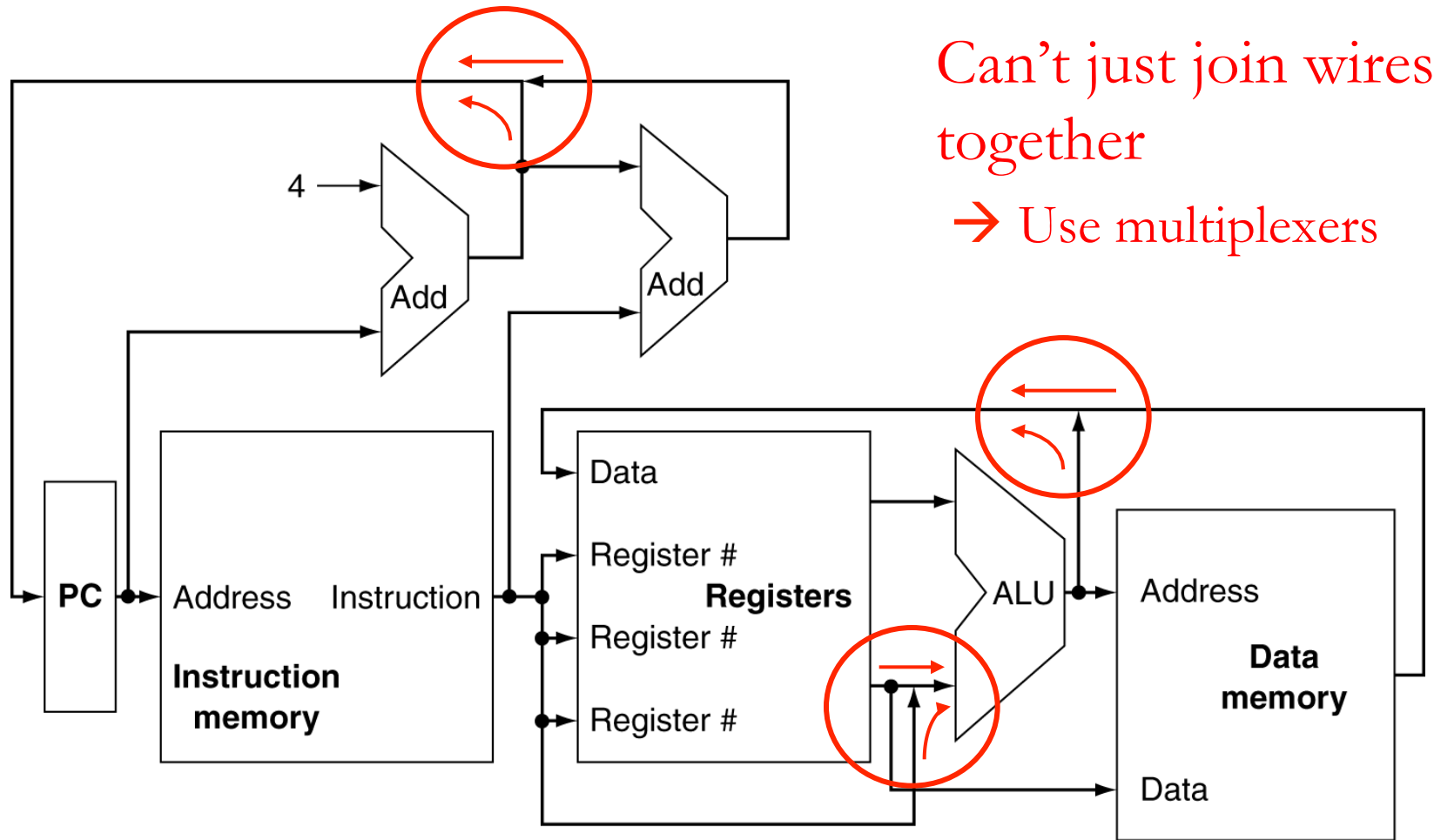


Full Datapath

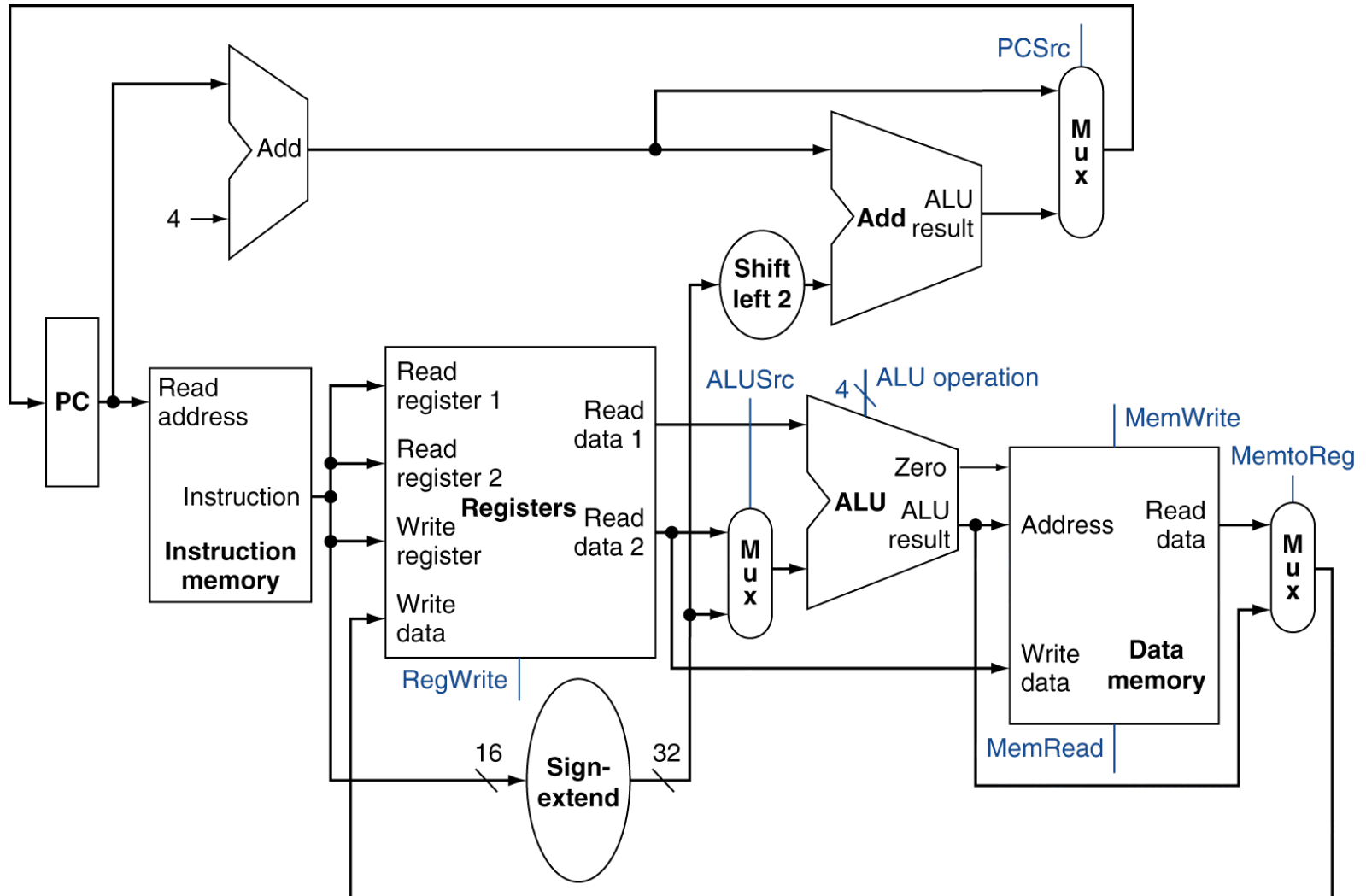


Full Datapath

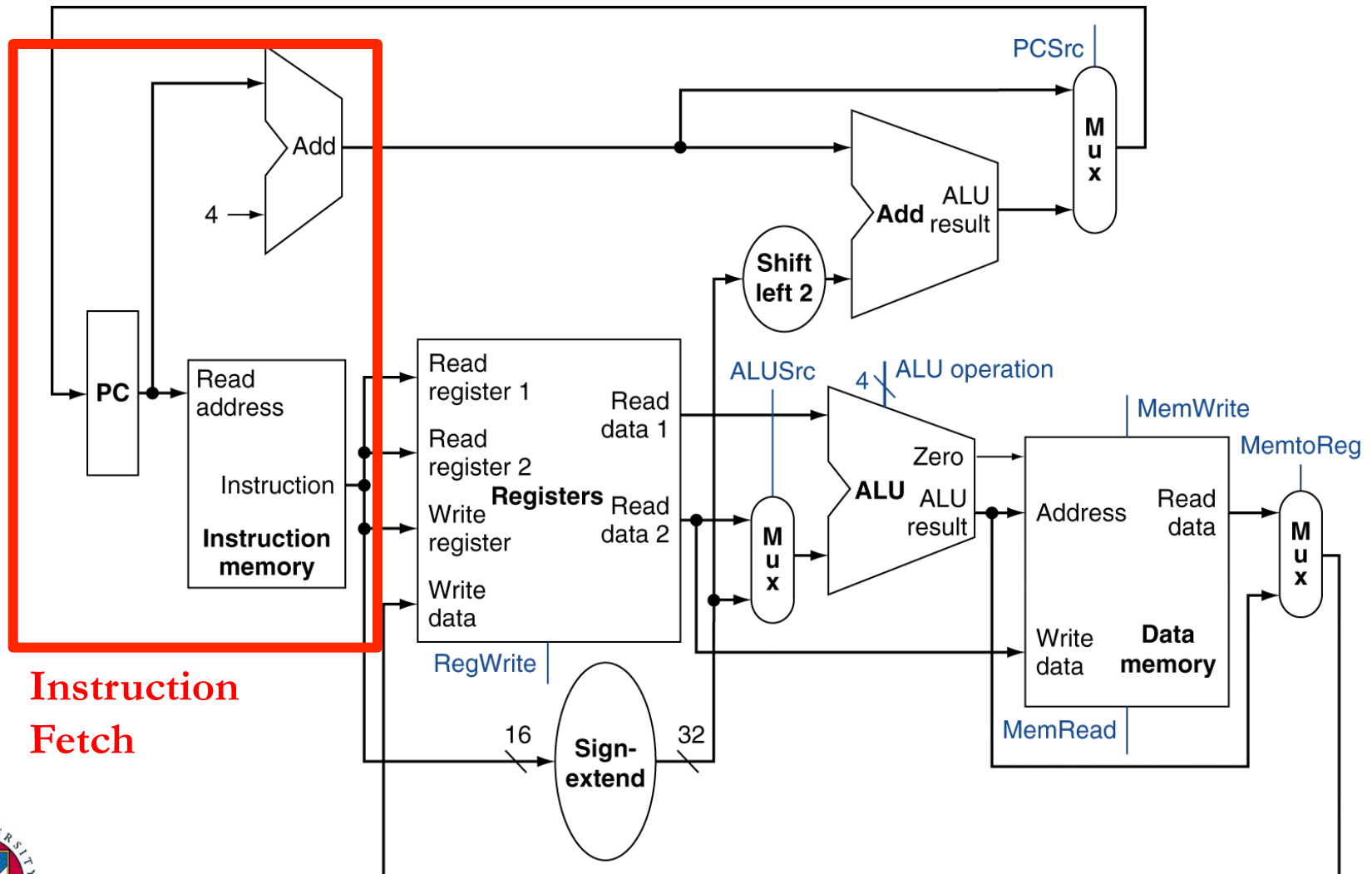

 

Full Datapath

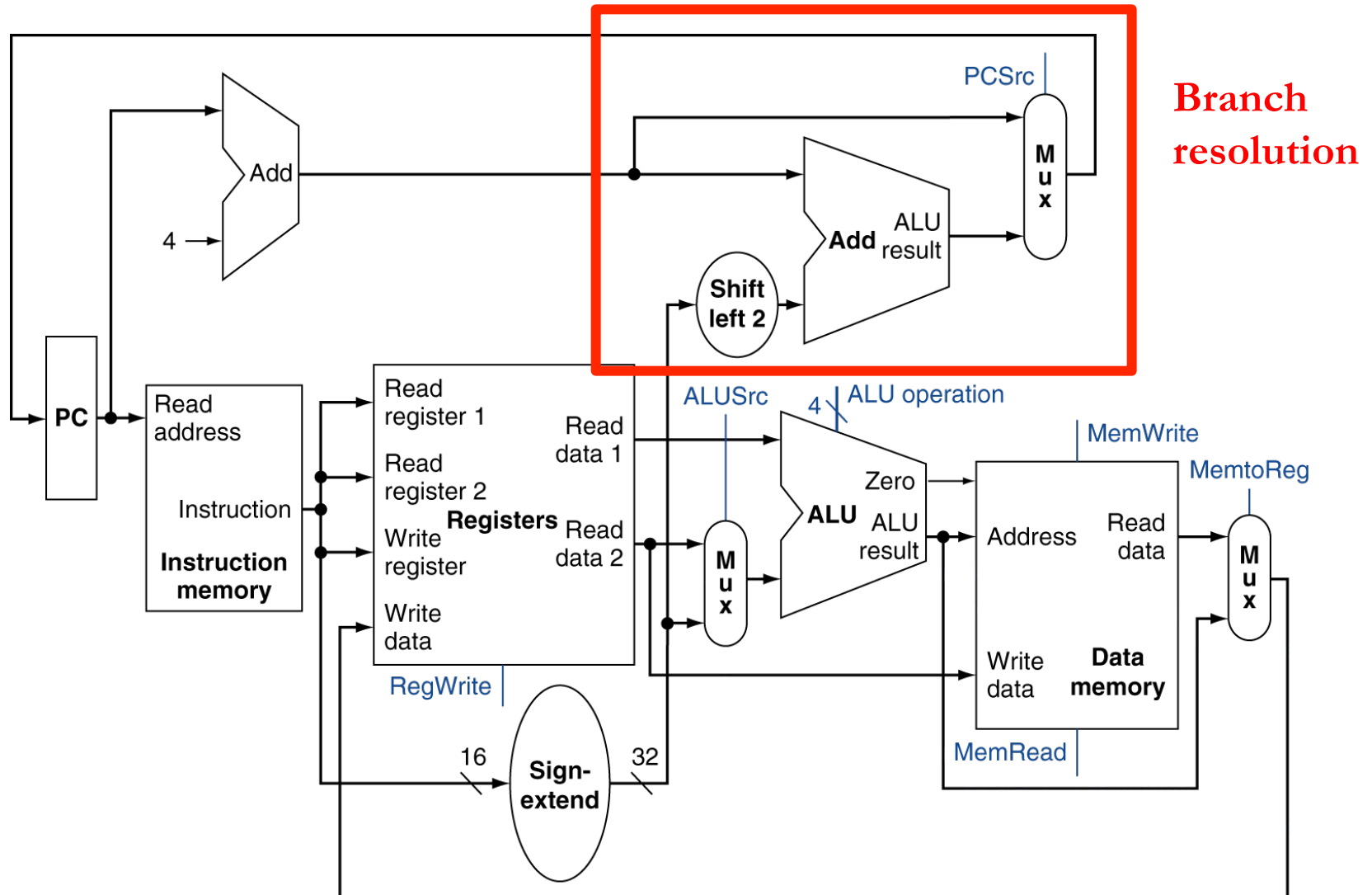


How to design the control part


- For all control signals determine which value selects what operation, input, etc.
- Make truth table of control signal values for each instruction, or instruction group
- Convert table to combinational circuit

Designing the Main Control Unit

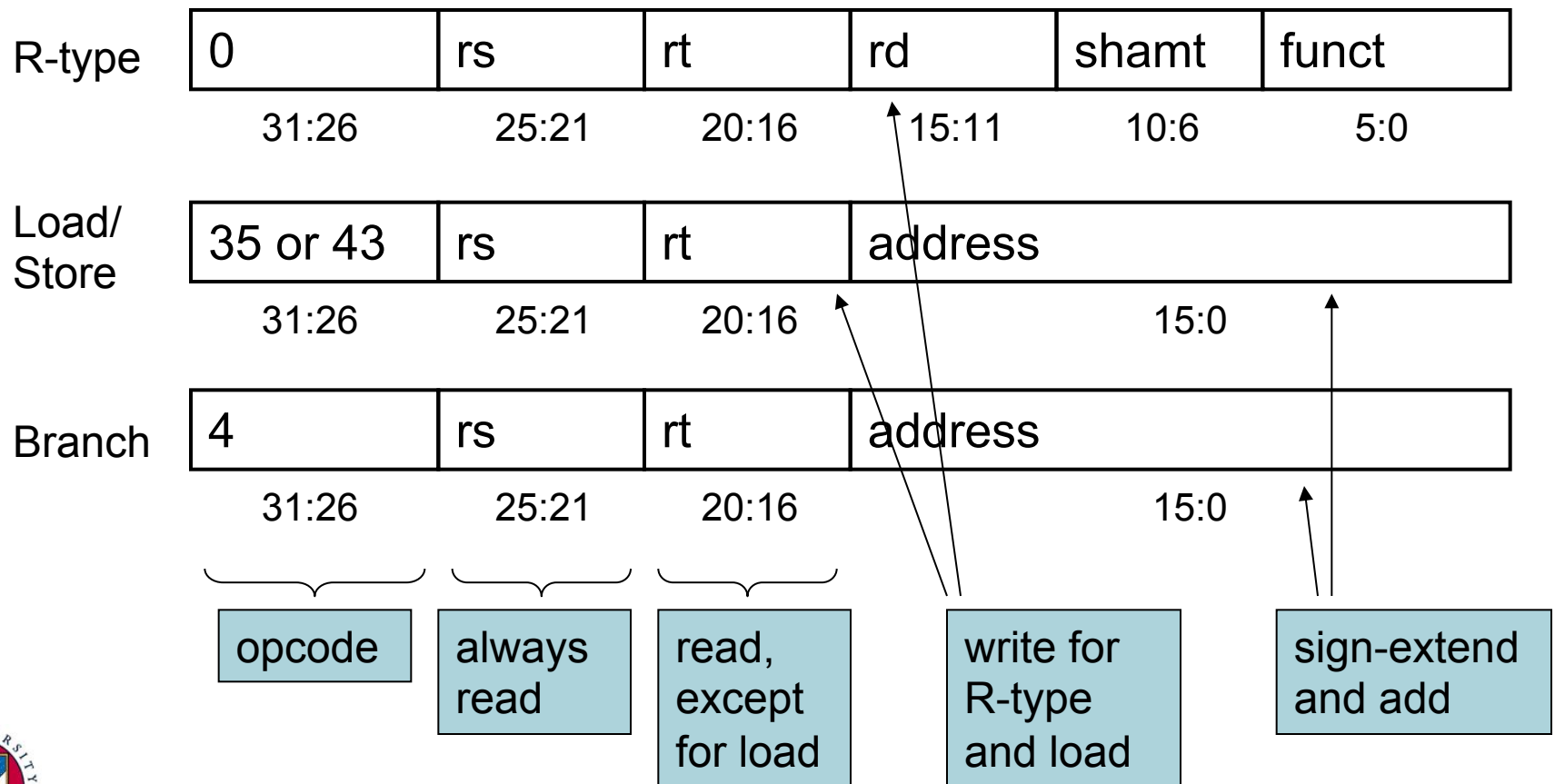
Control signals derived from instruction fields



Datapath with Control

 

Datapath and control truth table

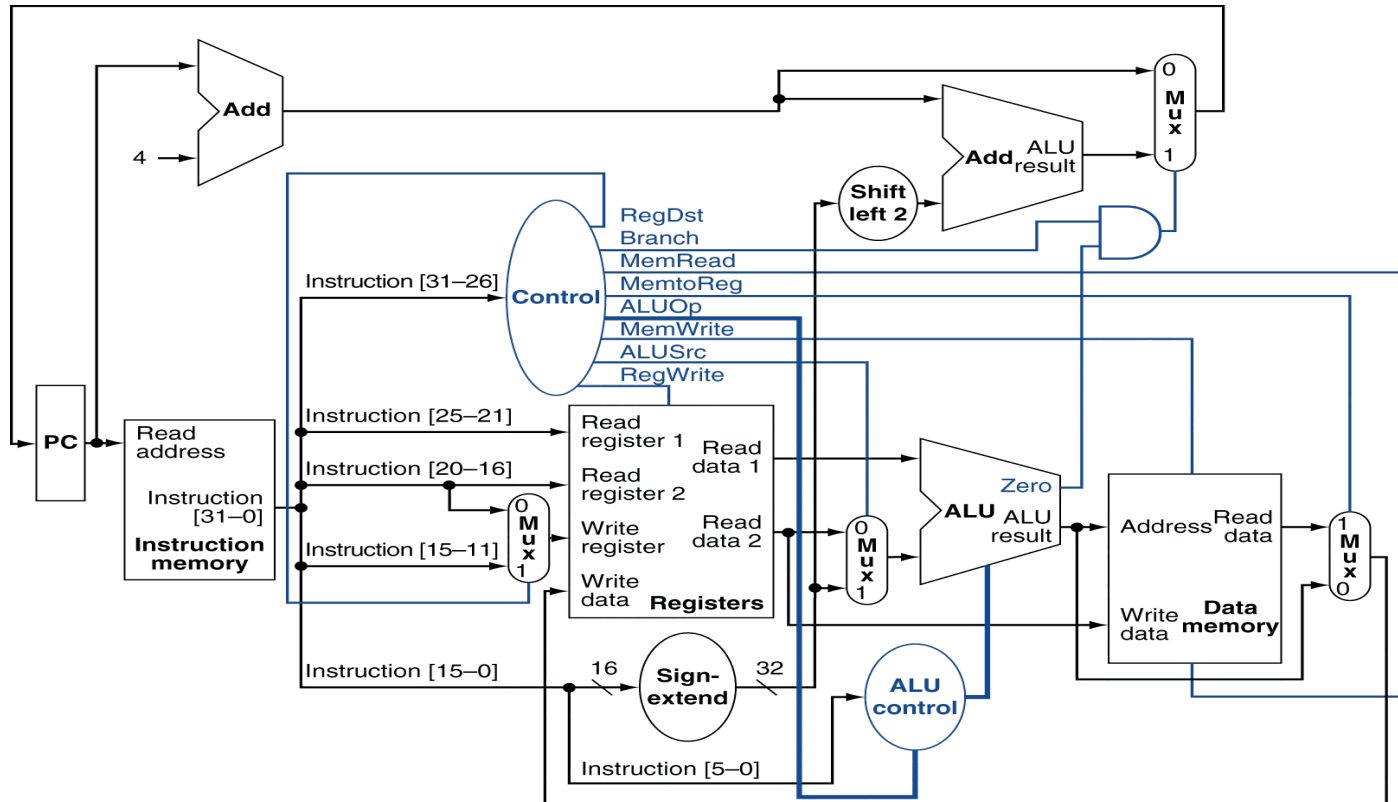

Instruction	RegDst	ALUSrc	Memto-Reg	Reg Write	Mem Read	Mem Write	Branch	ALUOp1	ALUOp0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1




Don't Care

ALU control

ALU operation:

 - Data transfers (ld/st) – add
 - Branches – sub
 - All other – determined by funct field, I[5:0]
- derived from opcode



ALU control


ALU control is **hierarchical**:

- Main control specifies which of the 3 op types
 - Add, Sub, or based on Funct bits
- Second level provides actual ALU control signal


ALU operation	
0000	AND
0001	OR
0010	add
0110	subtract
0111	set-on-less than

} actual
ALU Control
signals


R-type instruction execution

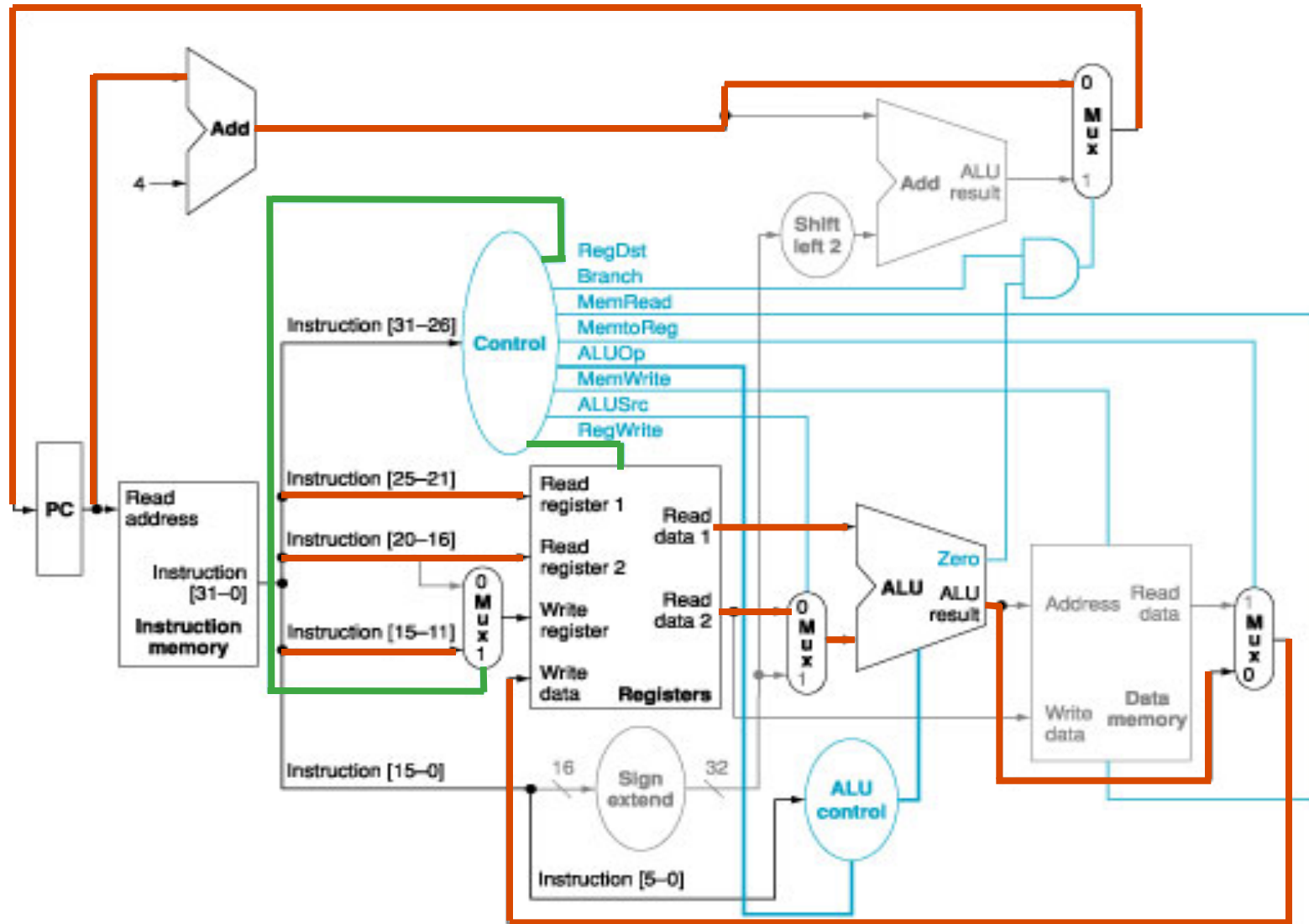

lw execution



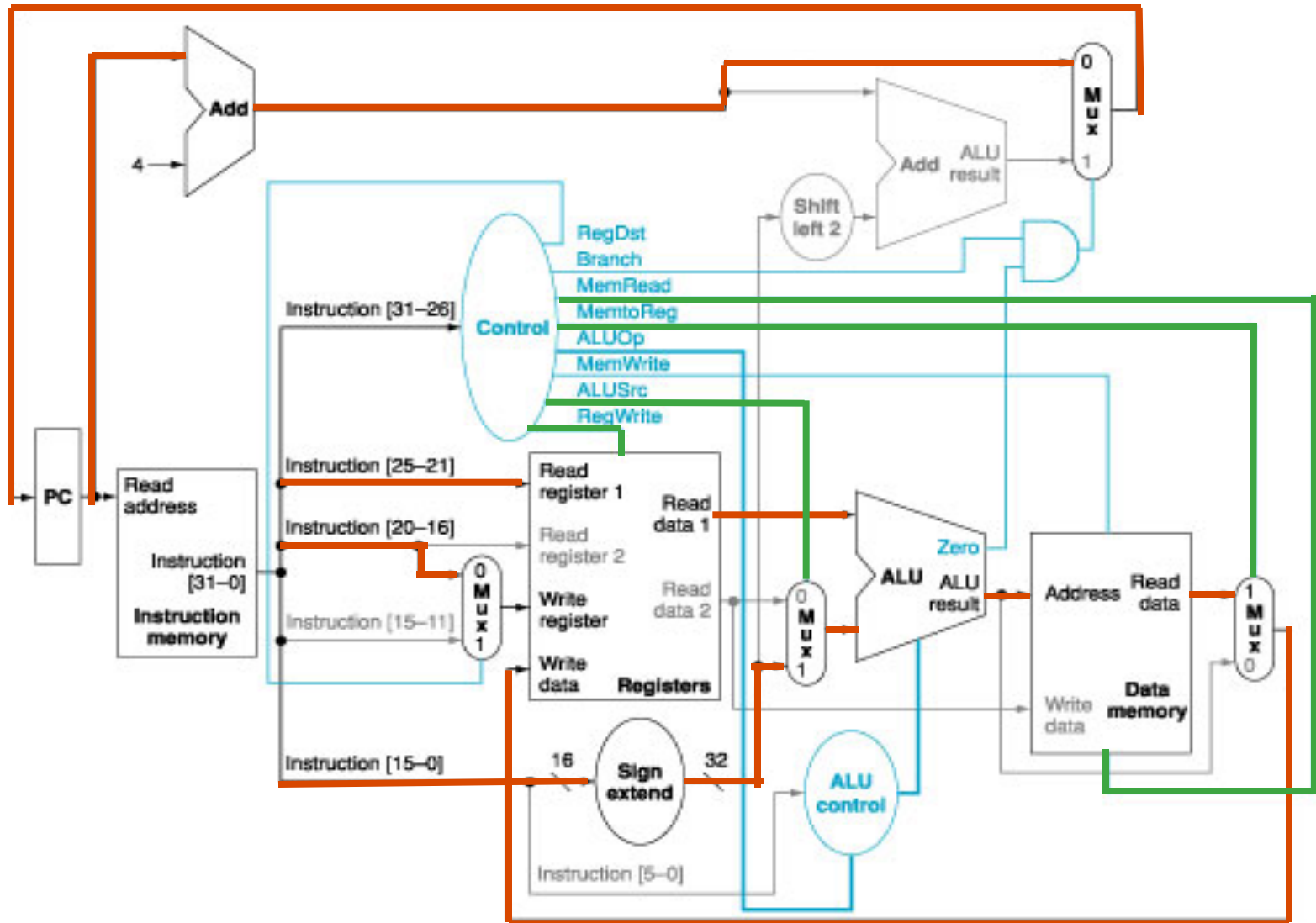


beq (taken) execution

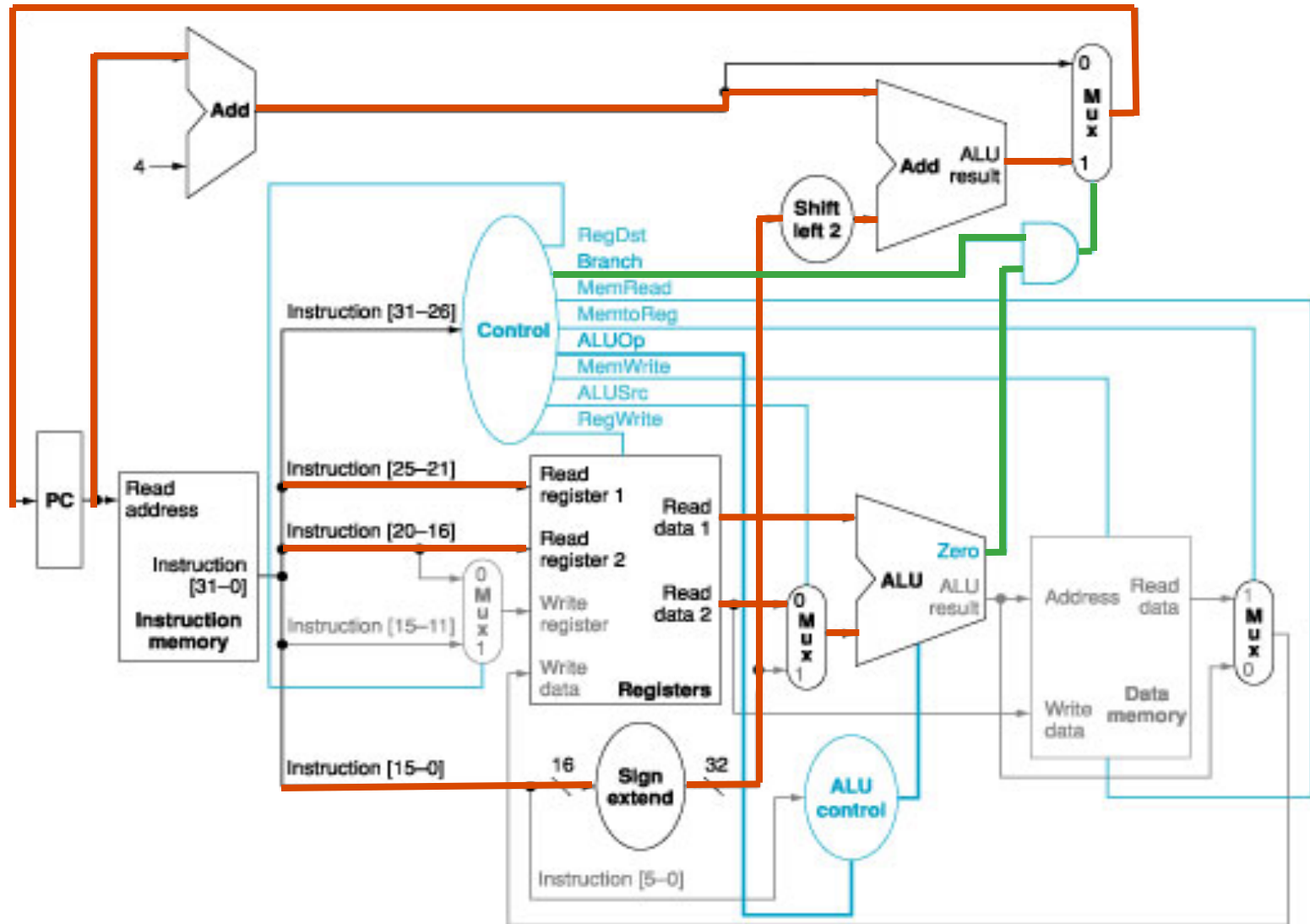

Don't fall behind!

   - Read the textbook (Chapter 4 in 4/e & 5/e)



- Multi-cycle datapath (Tues): on [Learn](#)
- Tutorials next week